

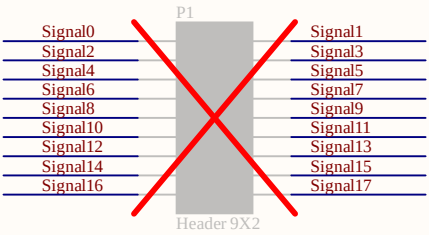
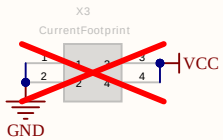
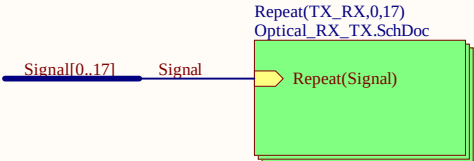


Connector
CarrierConnector.SchDoc

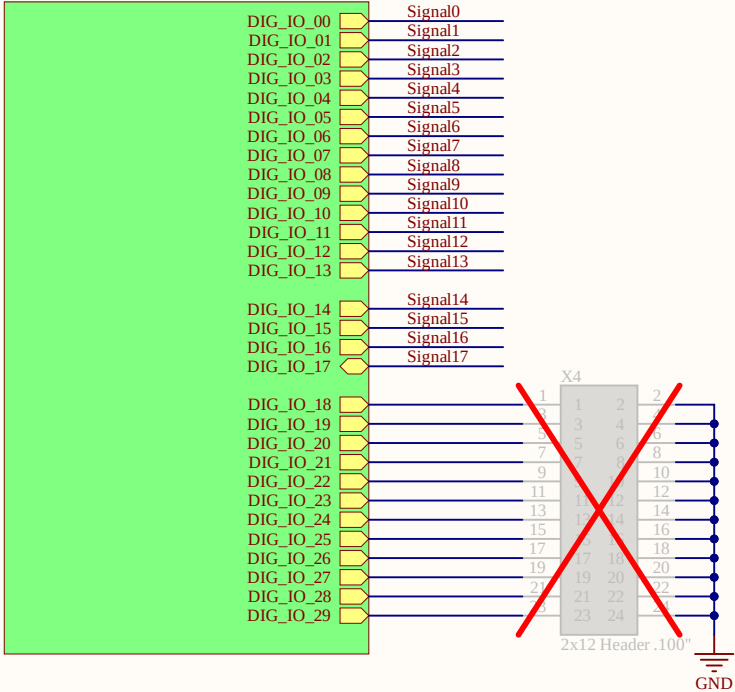

Serial1
Serial
Serialnumber 6,3 x 6.3mm

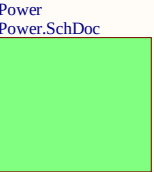ProjectName1
Laser1
Logo Laser
Voll_Laser



A

A

B



B

C

C


D

D

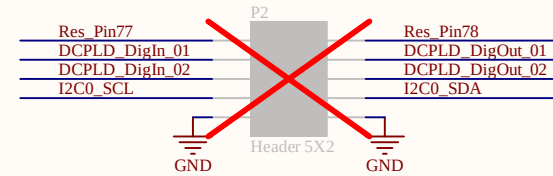
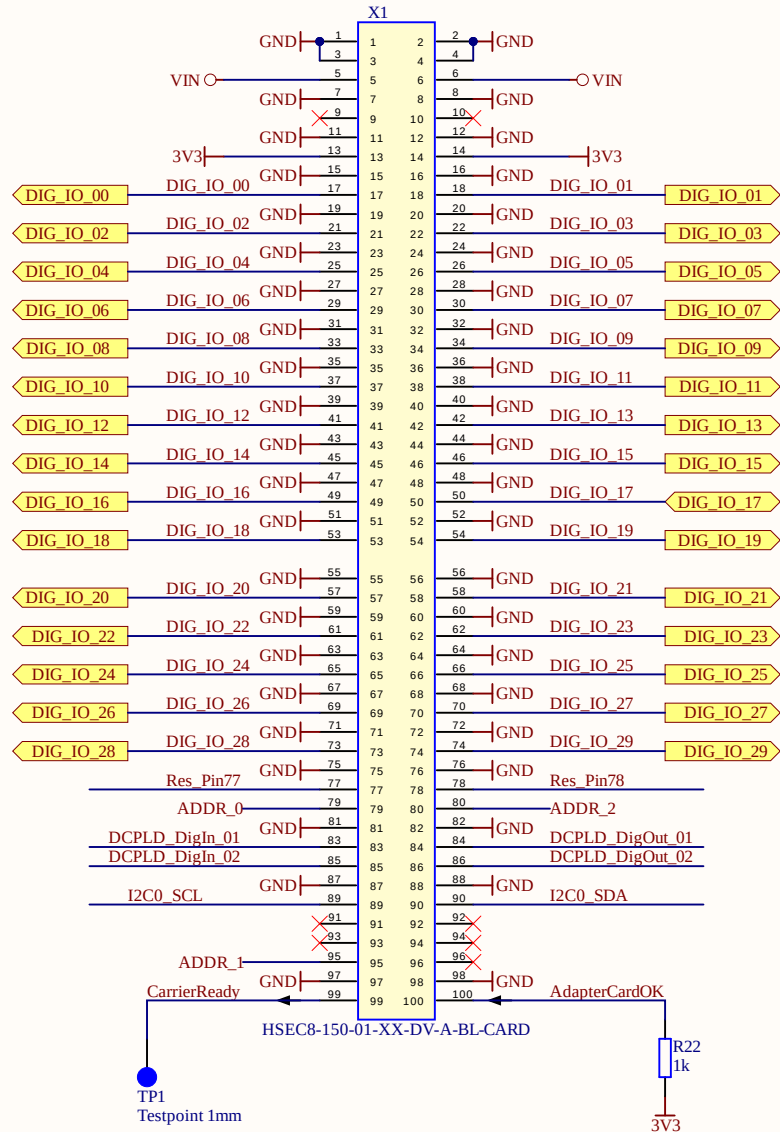


EEPROM

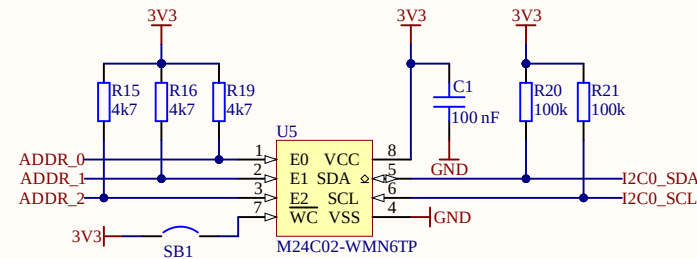This EEPROM enables the plugged-in adapter card to be identified by software. Leave this part in your design.



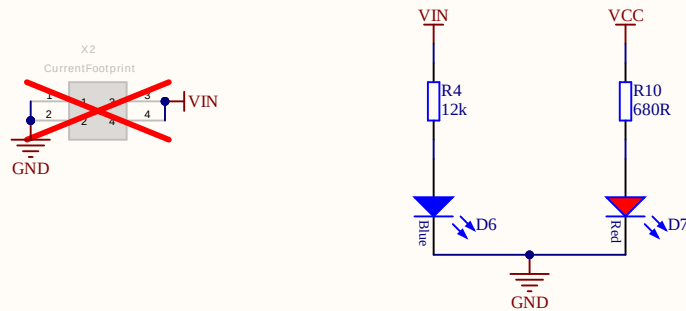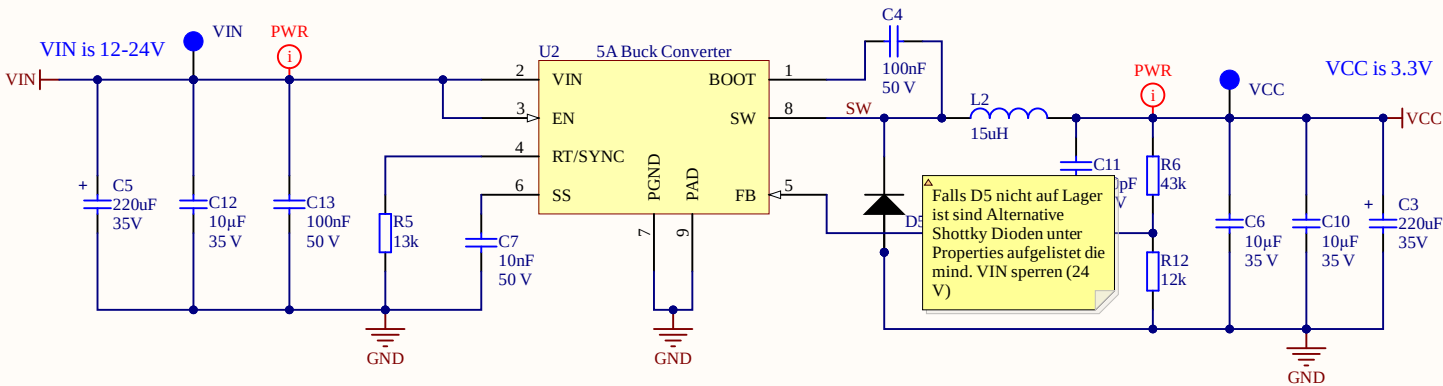Note: place solder bump to protect EEPROM memory from write access.




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

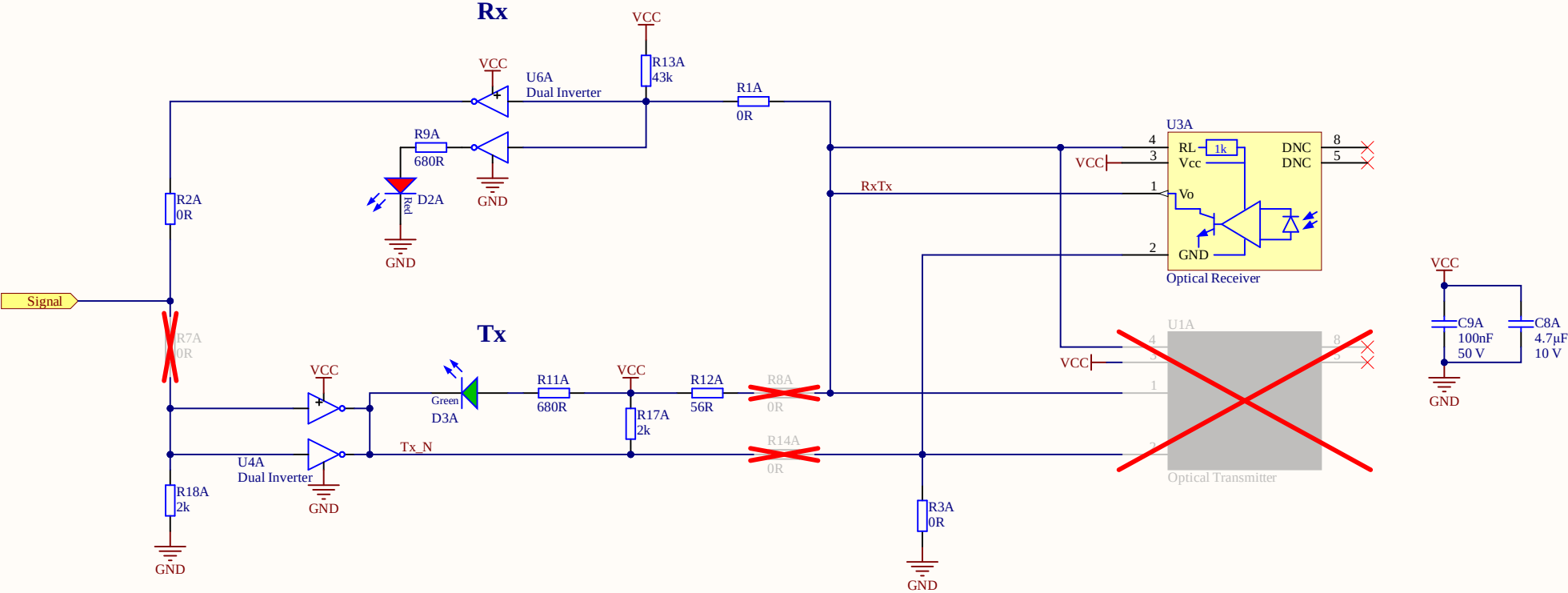

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.0 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

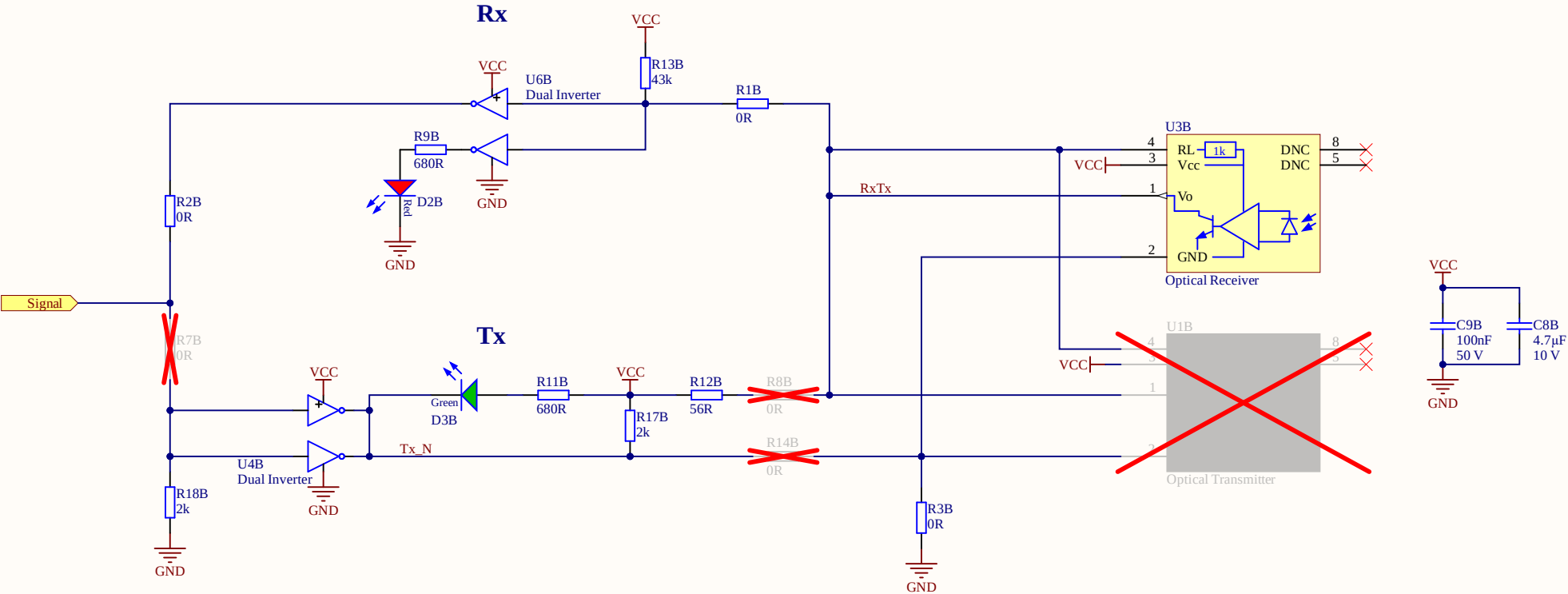

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.1 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

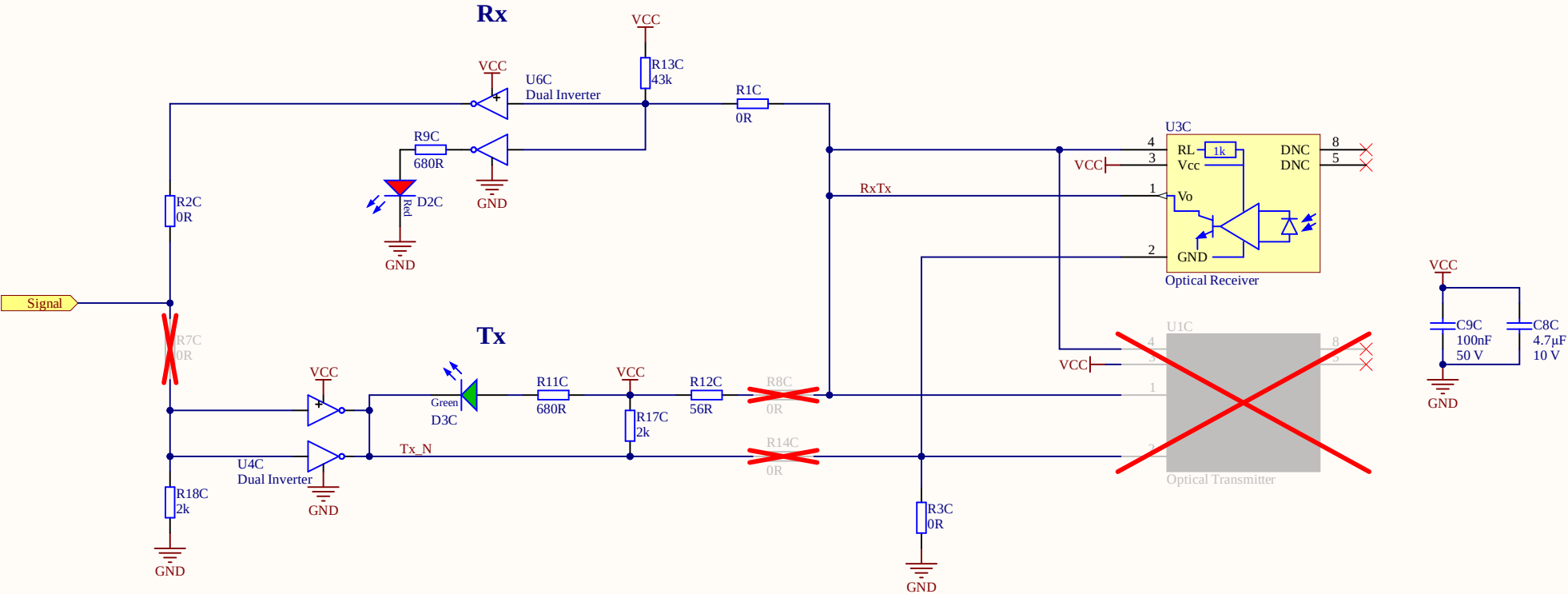

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.2 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

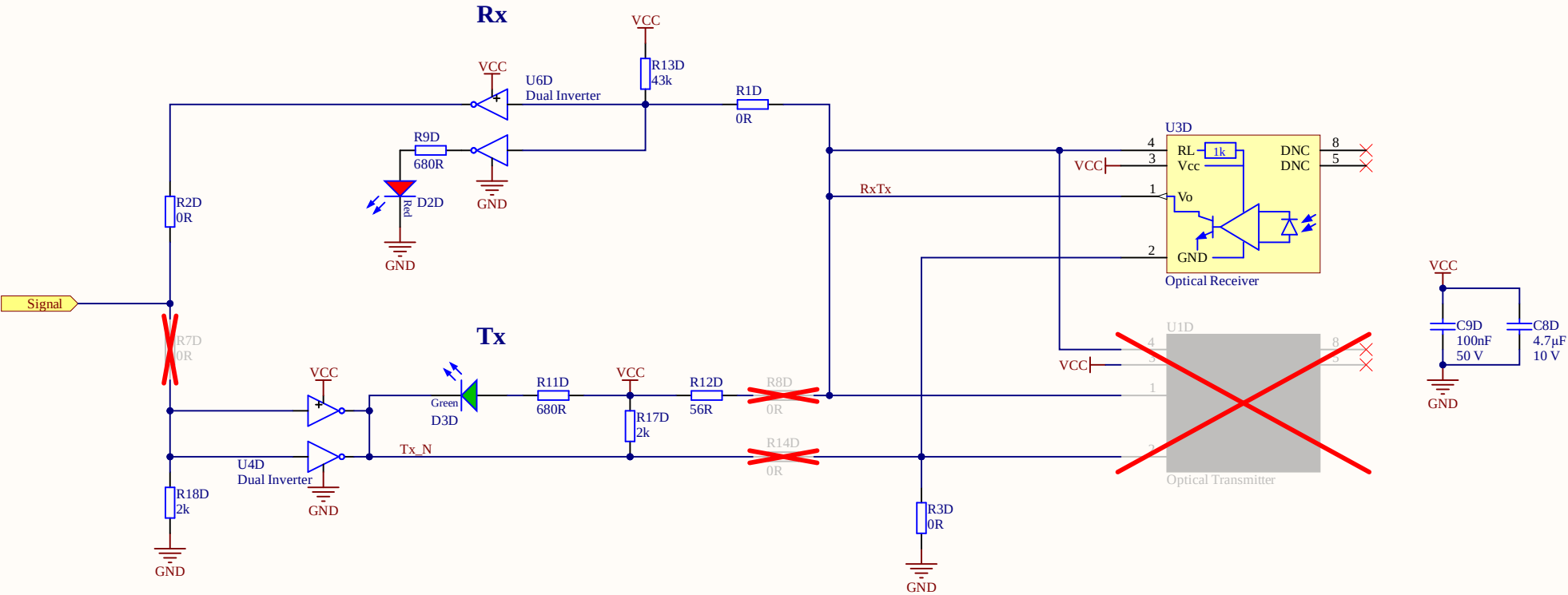


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

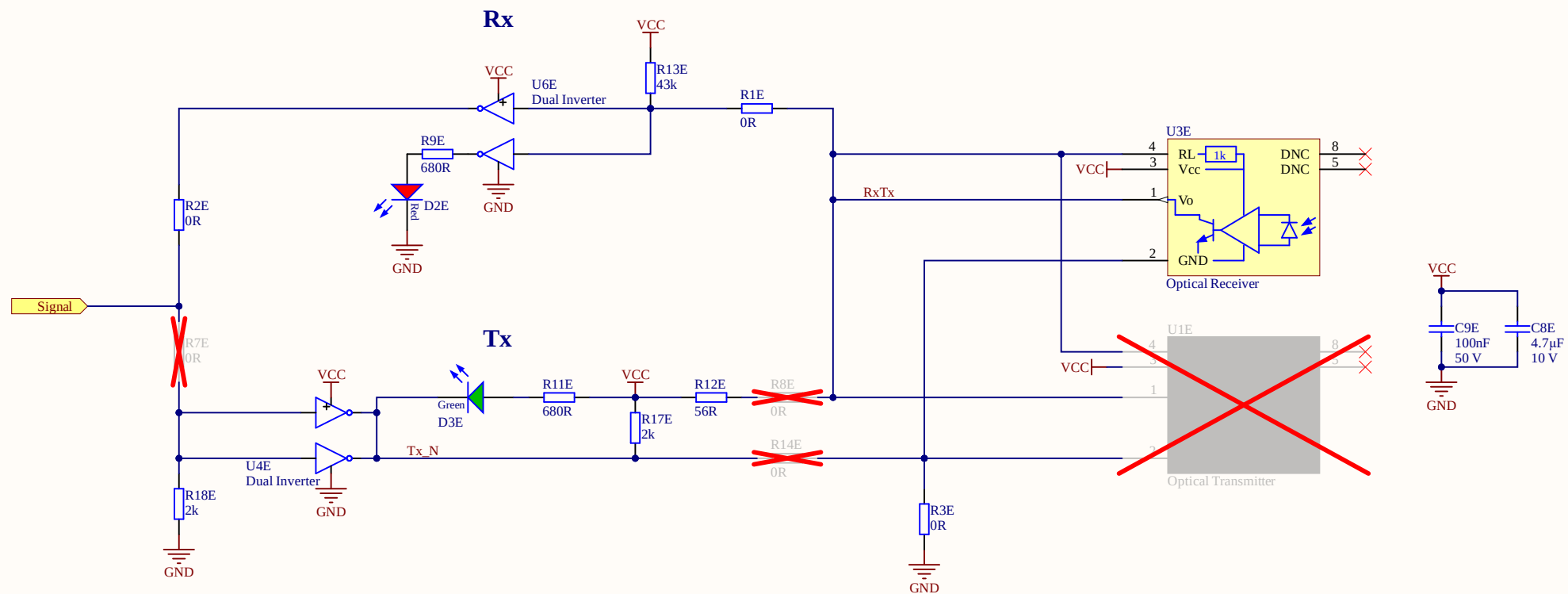

Title Optical_RX_TX.SchDoc	
Revision: Rev08	Design Engineer: B. Kohlmann & A.Geiger
Project: Digital_Optical.PrjPCB	




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

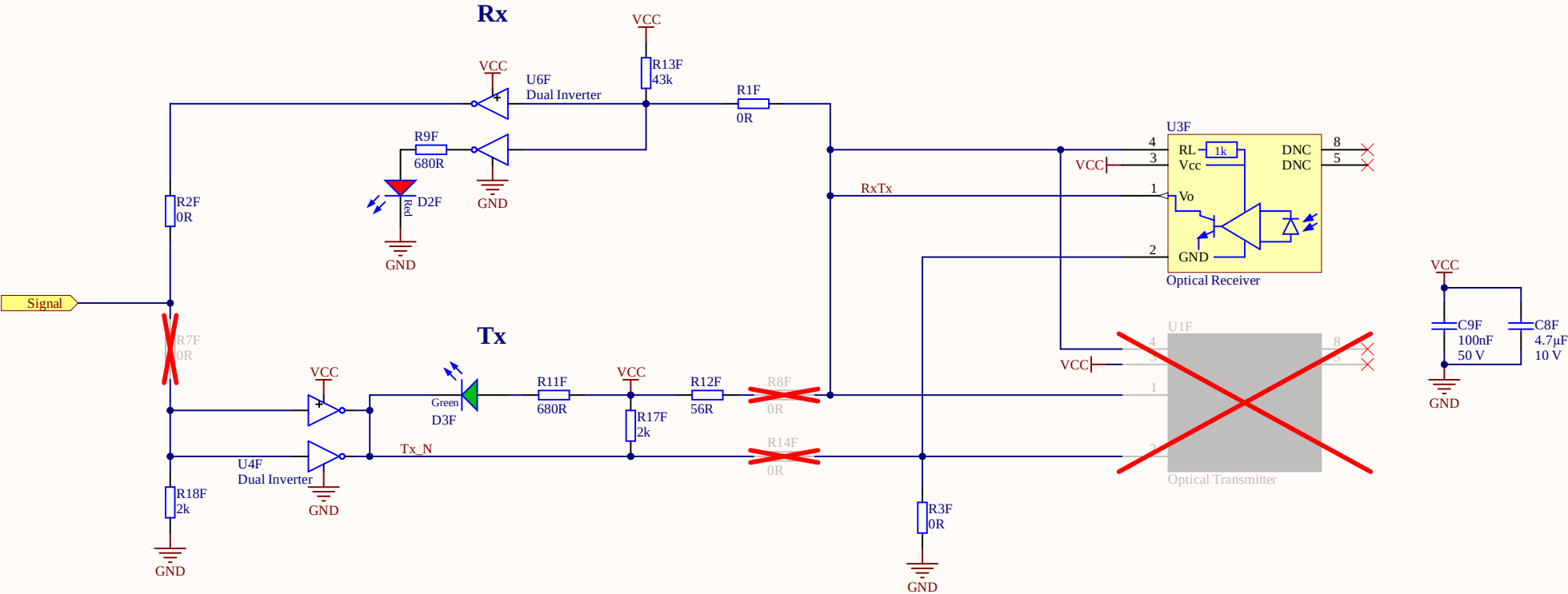

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.5 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

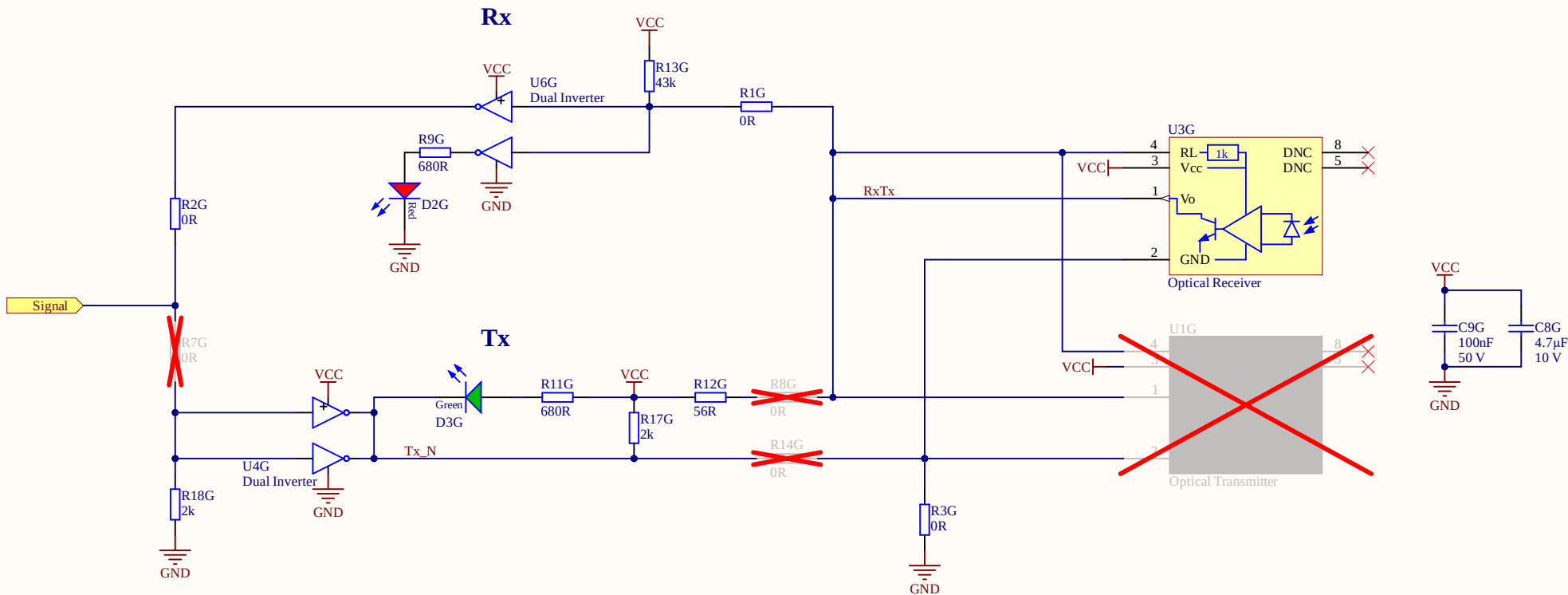

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.6 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

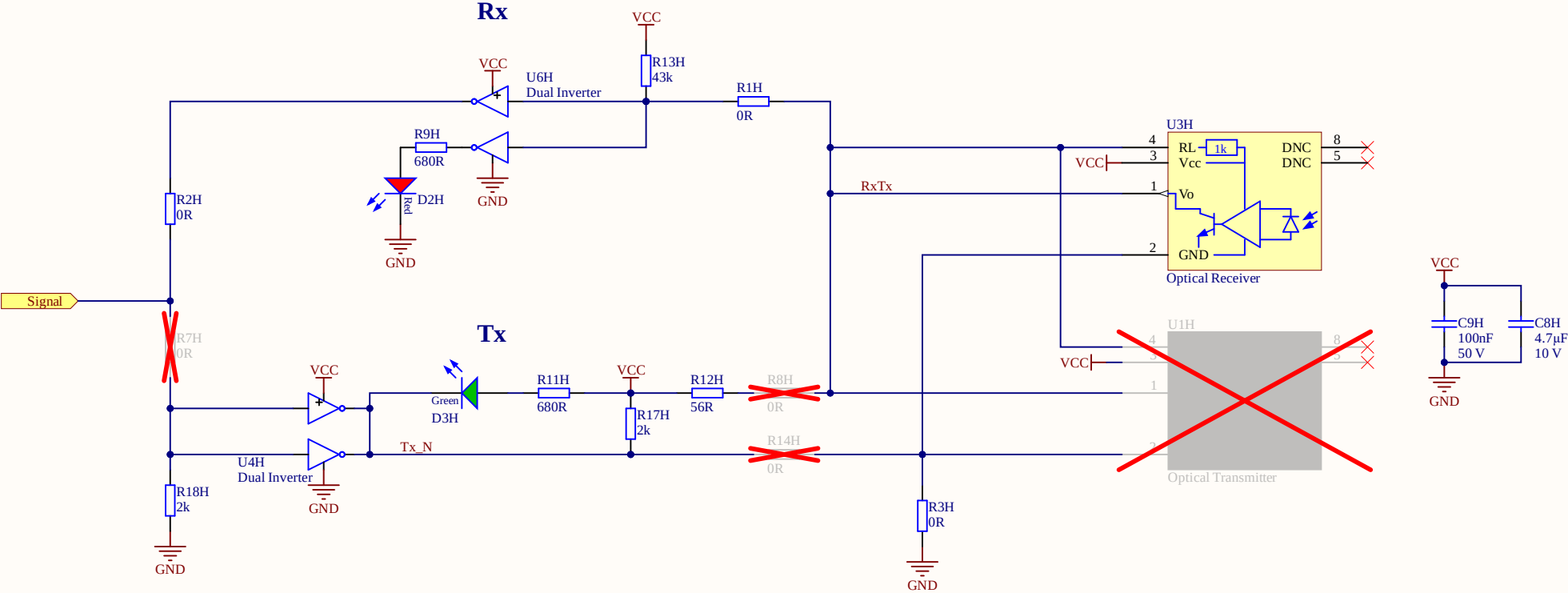


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

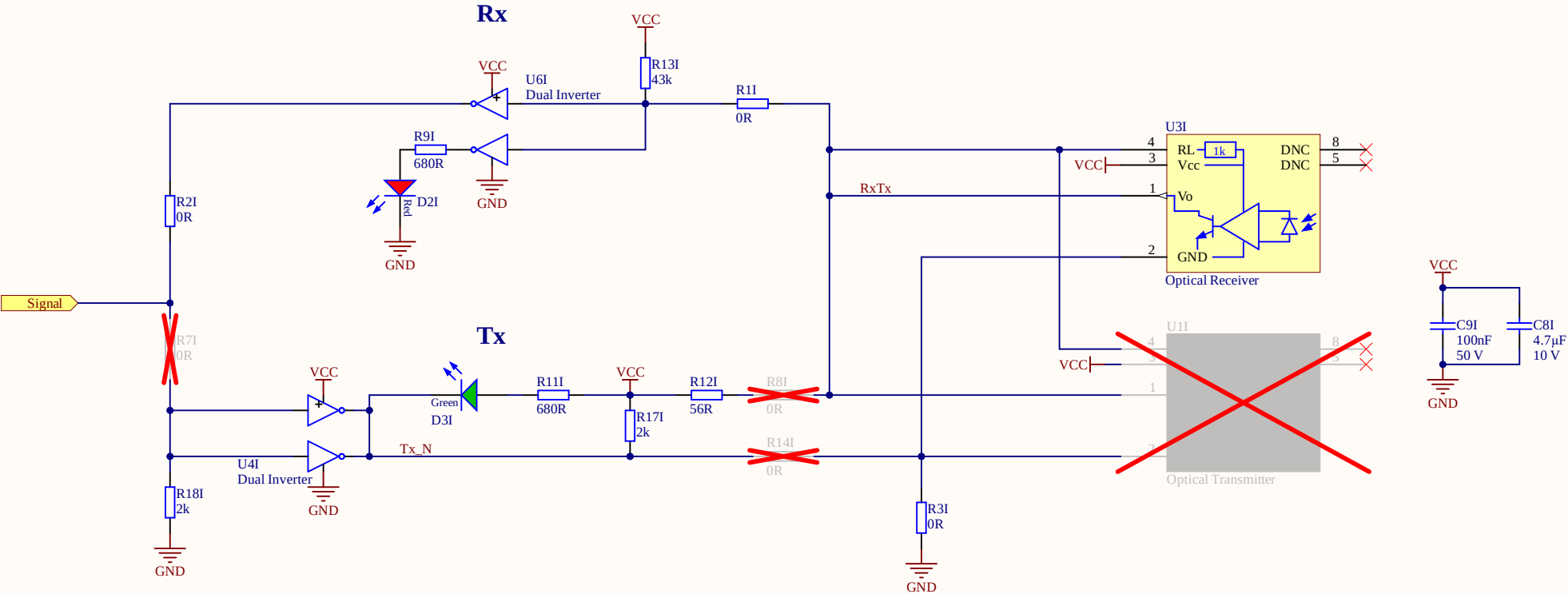

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.8 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

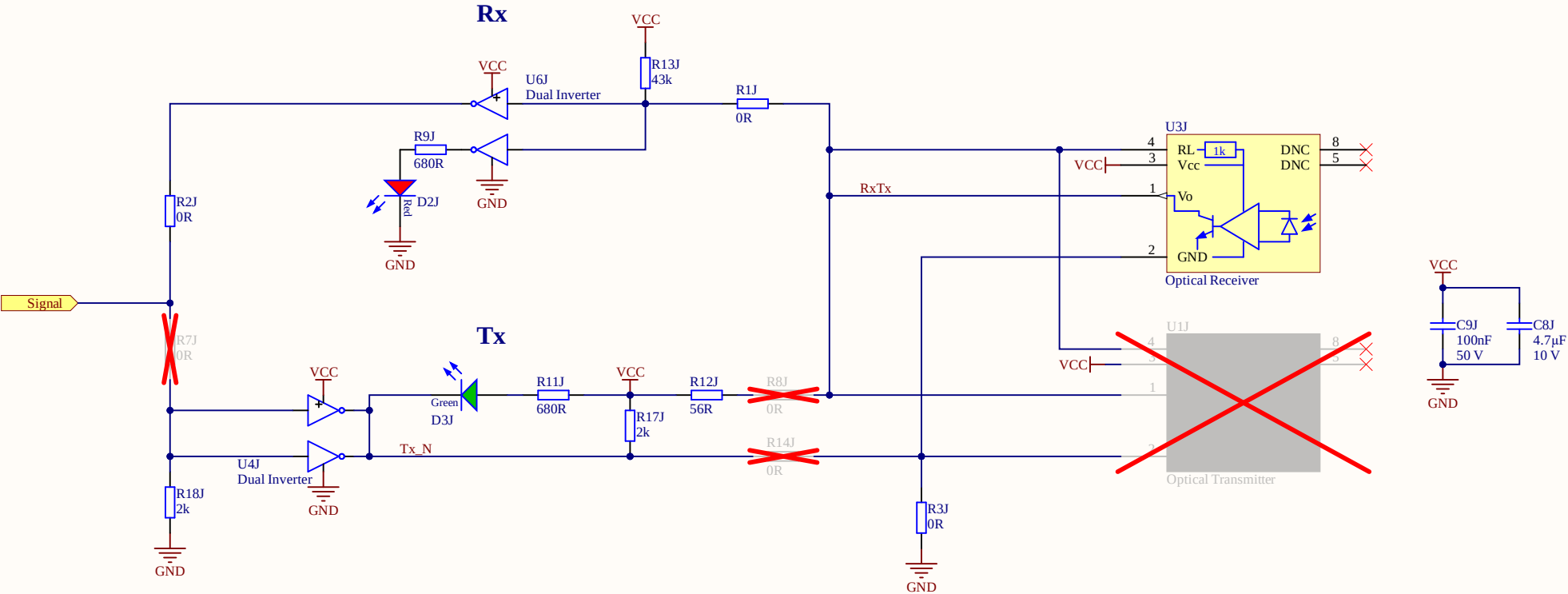

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.9 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

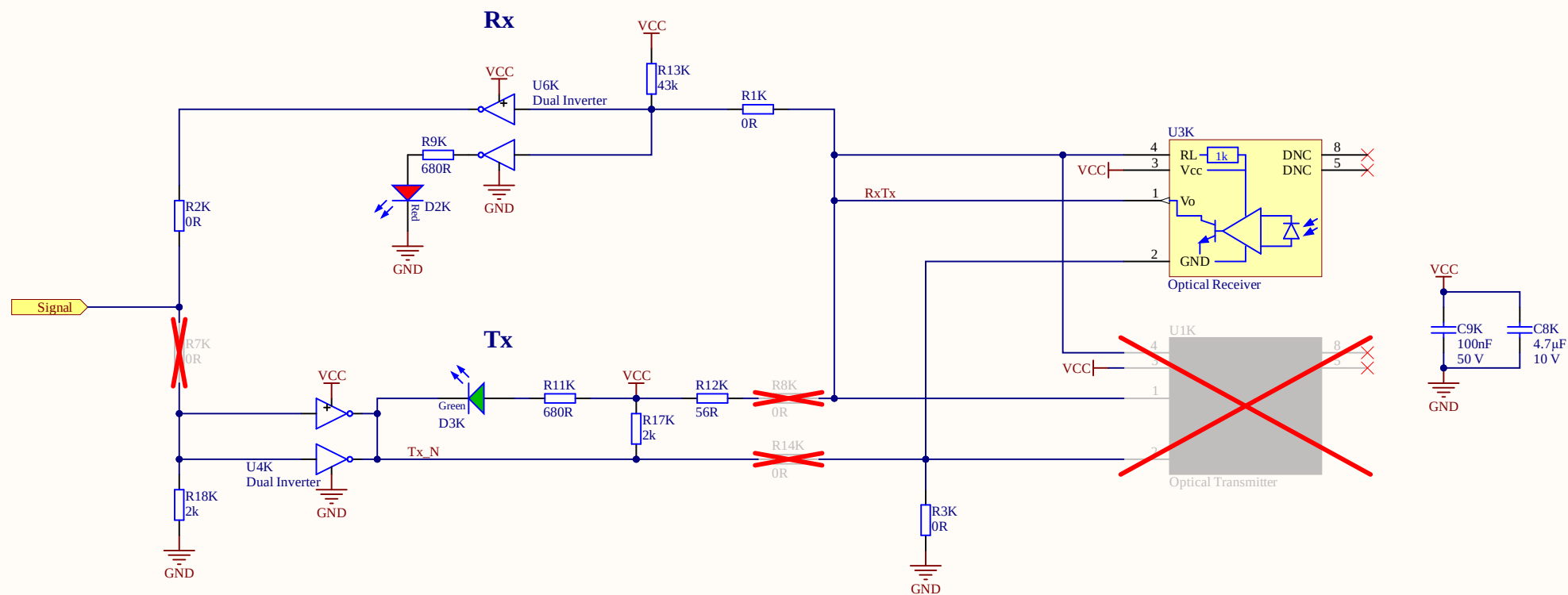

Title: Optical_RX_TX.SchDoc	
Revision: Rev08	Design Engineer: B. Kohlmann & A.Geiger
Project: Digital_Optical.PrjPCB	




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

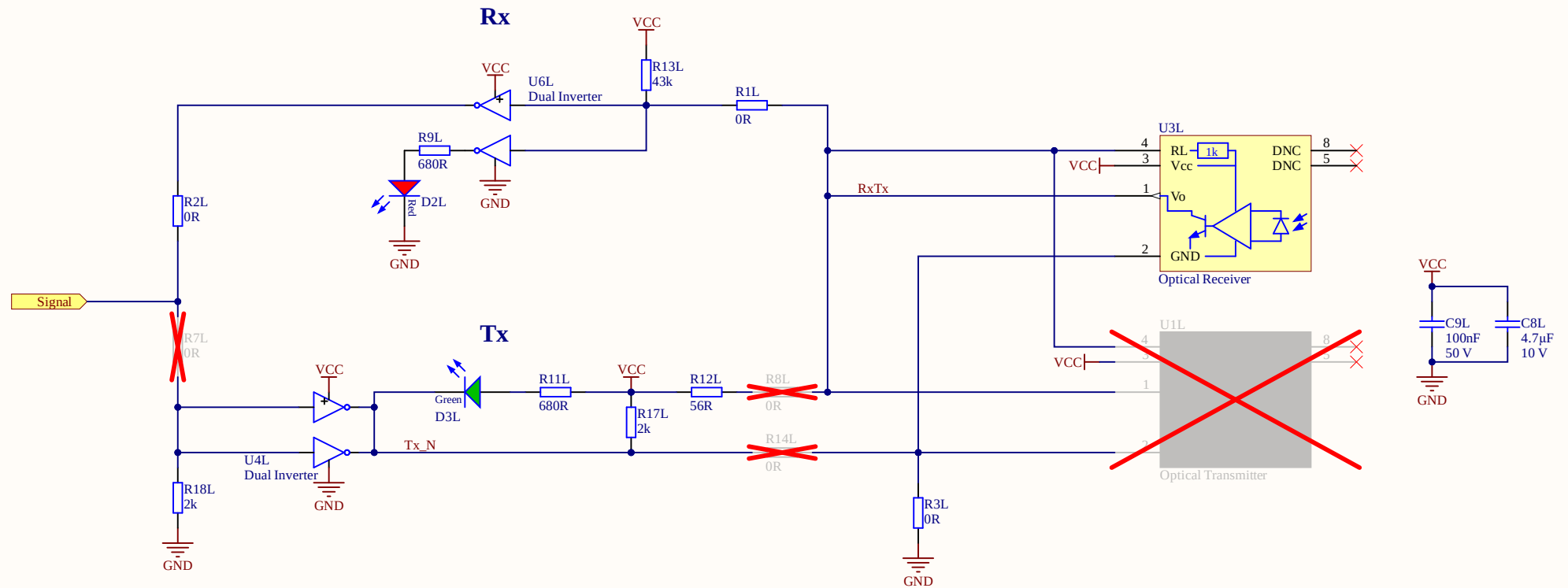

Title: Optical_RX_TX.SchDoc	
Revision: Rev08	Design Engineer: B. Kohlmann & A.Geiger
Project: Digital_Optical.PrjPCB	




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

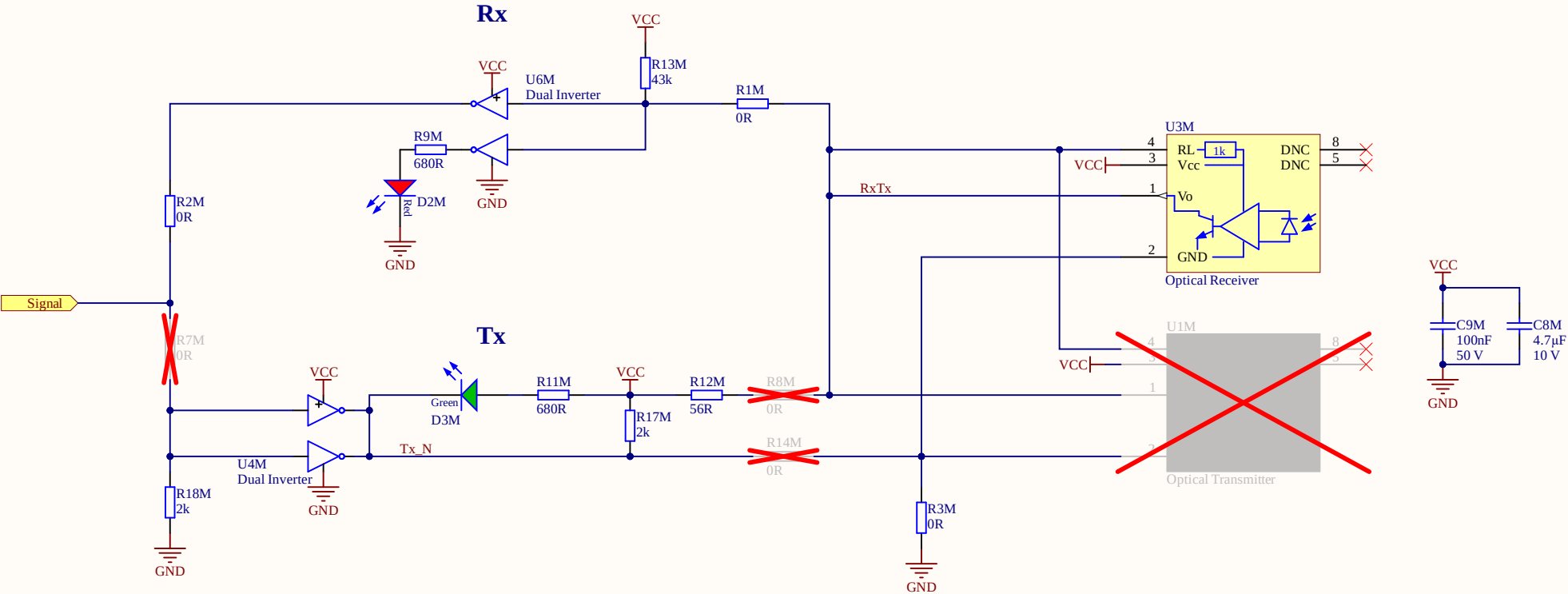

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.12bf 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

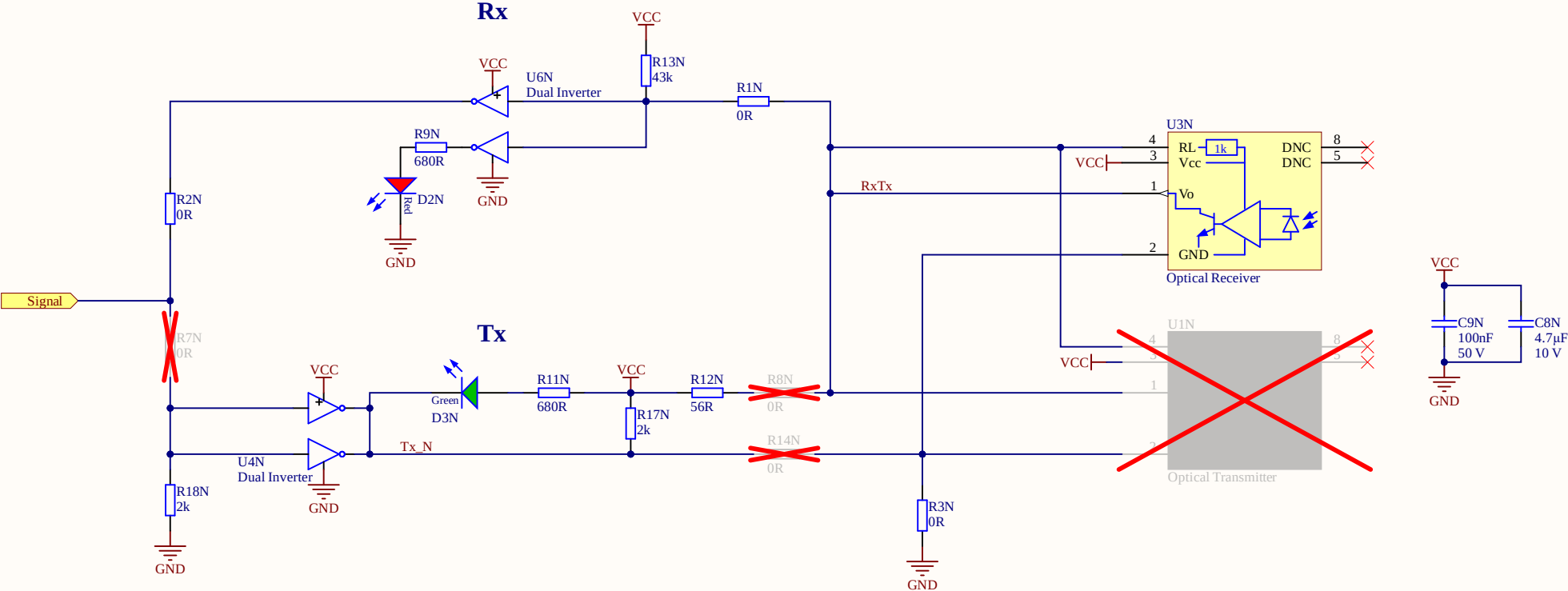


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

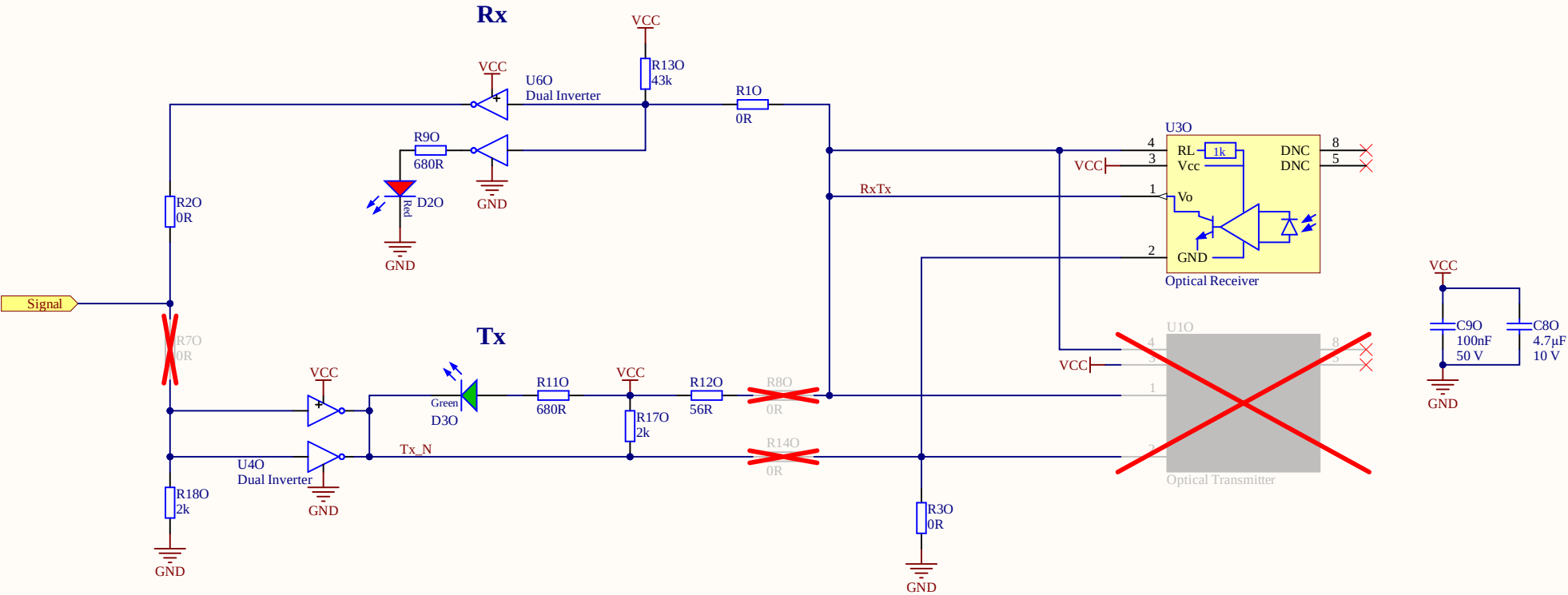


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

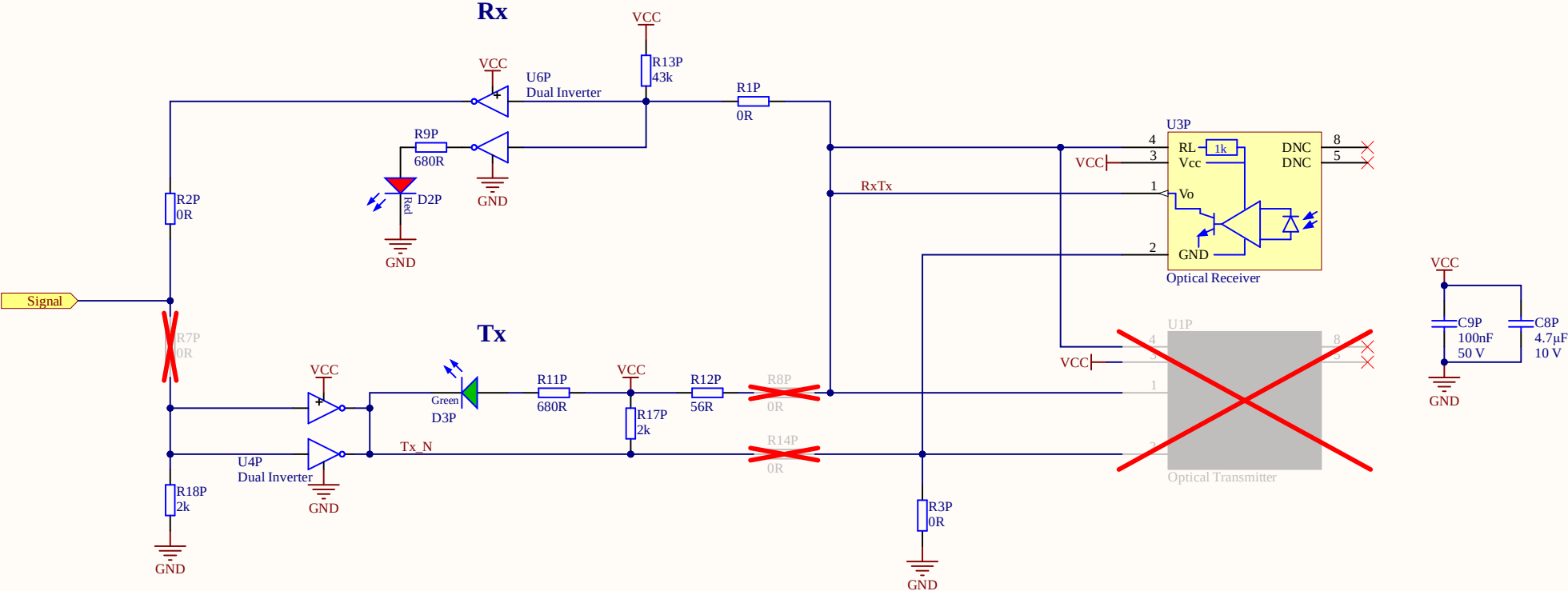

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.15of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

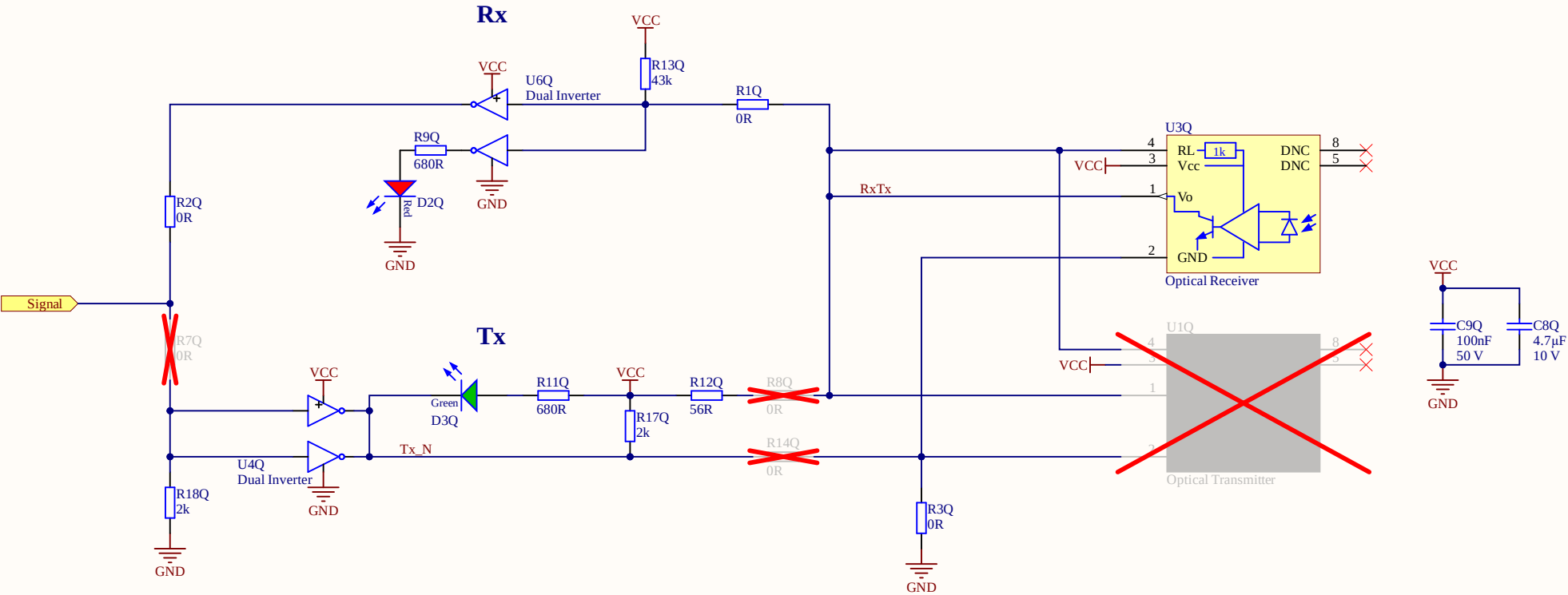

Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

