

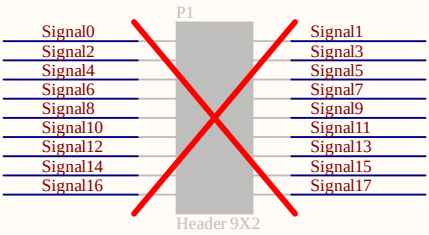
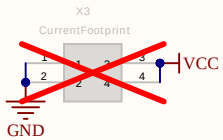
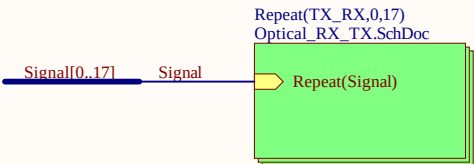




Connector
CarrierConnector.SchDoc

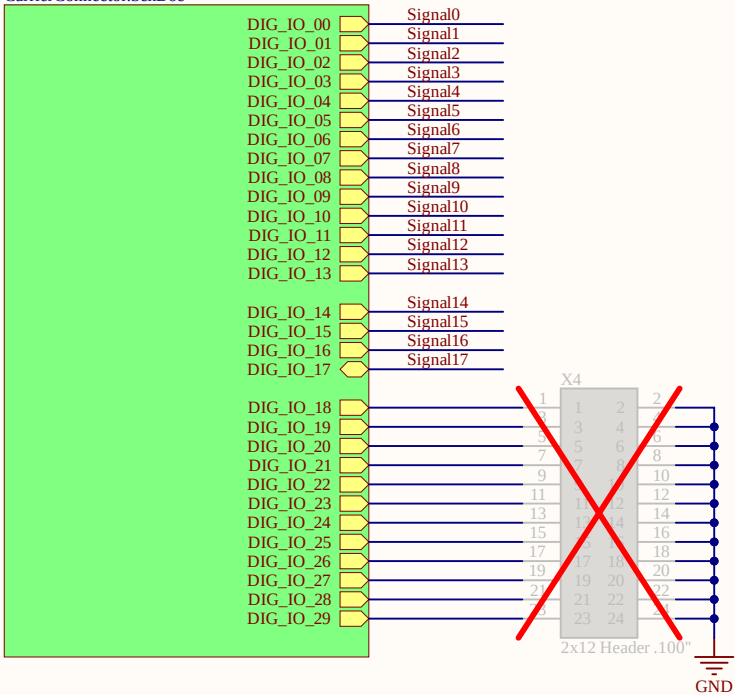

Serial1
Serial
Serialnumber 6,3 x 6.3mm

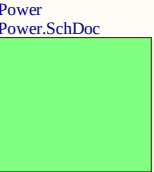
ProjectName1
Laser1
Logo Laser
Voll_Laser



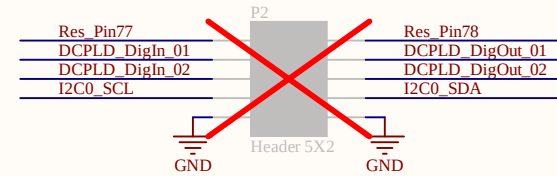
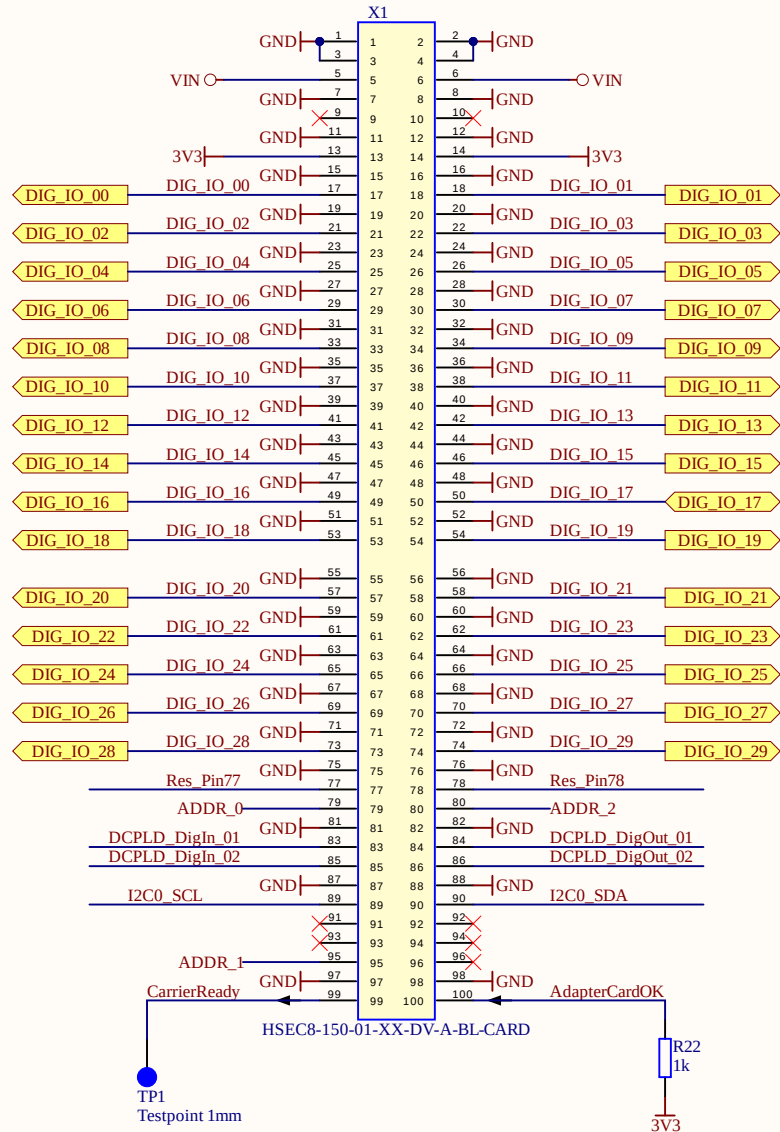


EEPROM

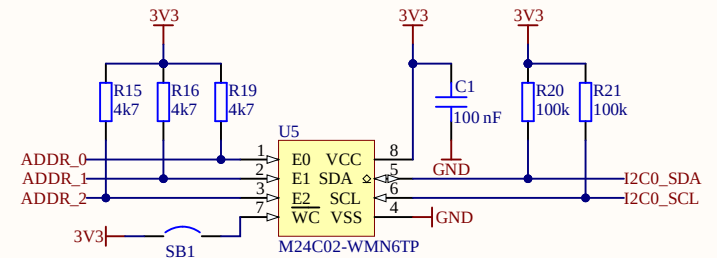This EEPROM enables the plugged-in adapter card to be identified by software. Leave this part in your design.



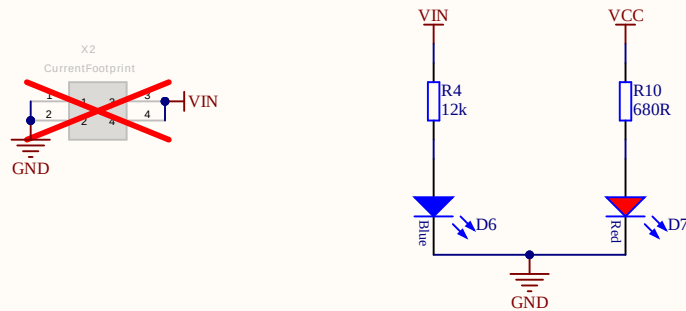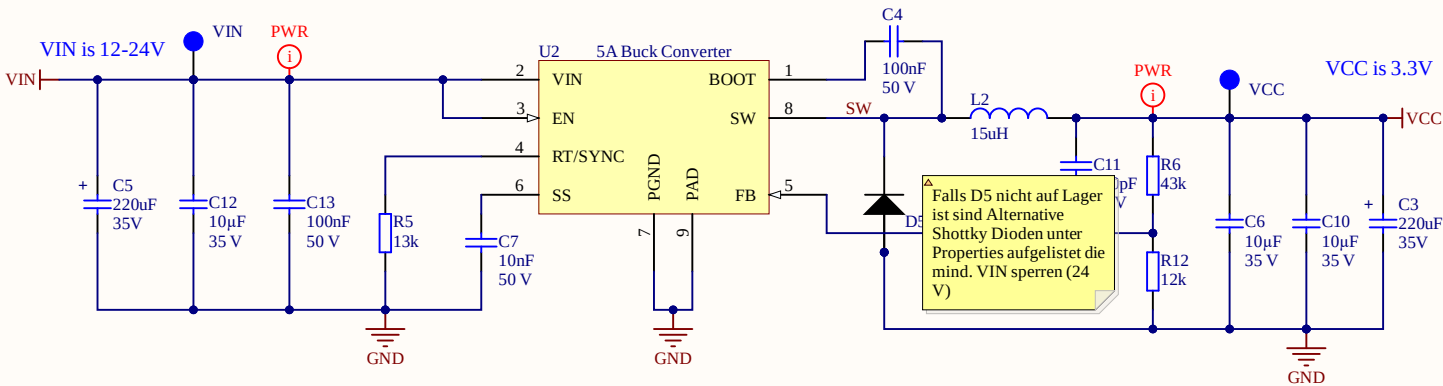Note: place solder bump to protect EEPROM memory from write access.




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

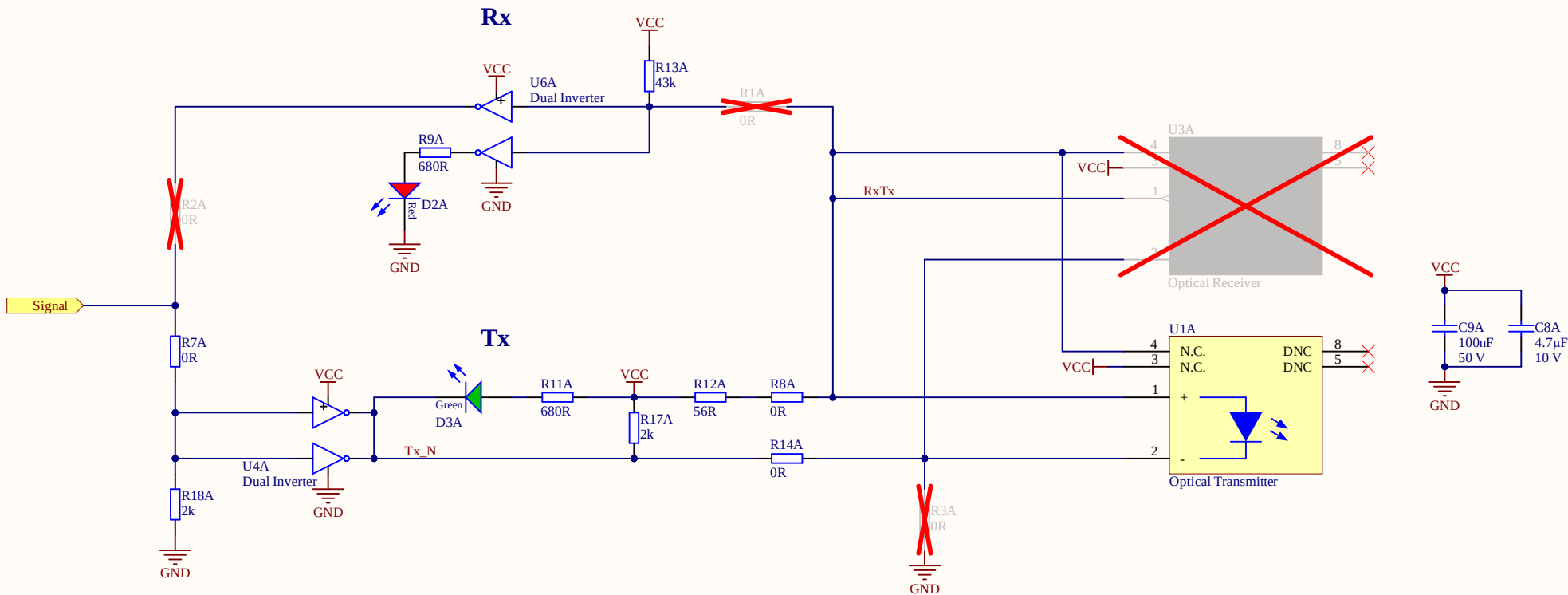


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

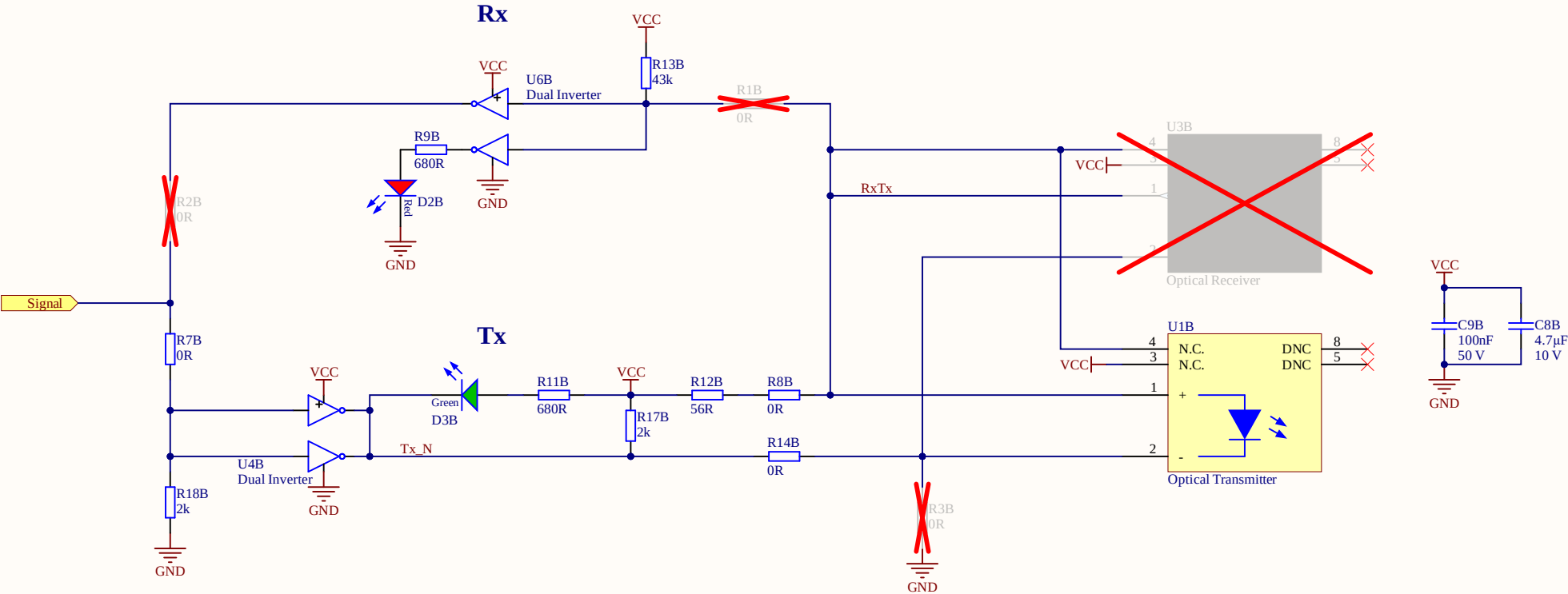


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

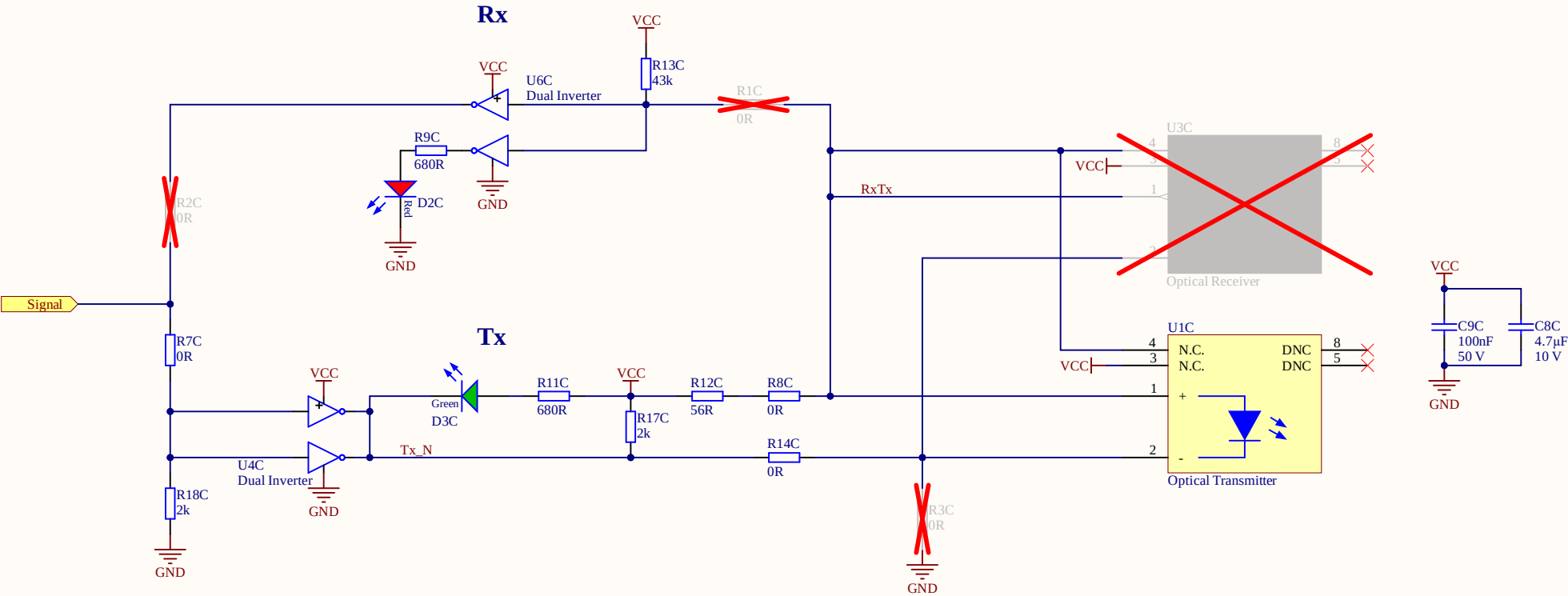


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

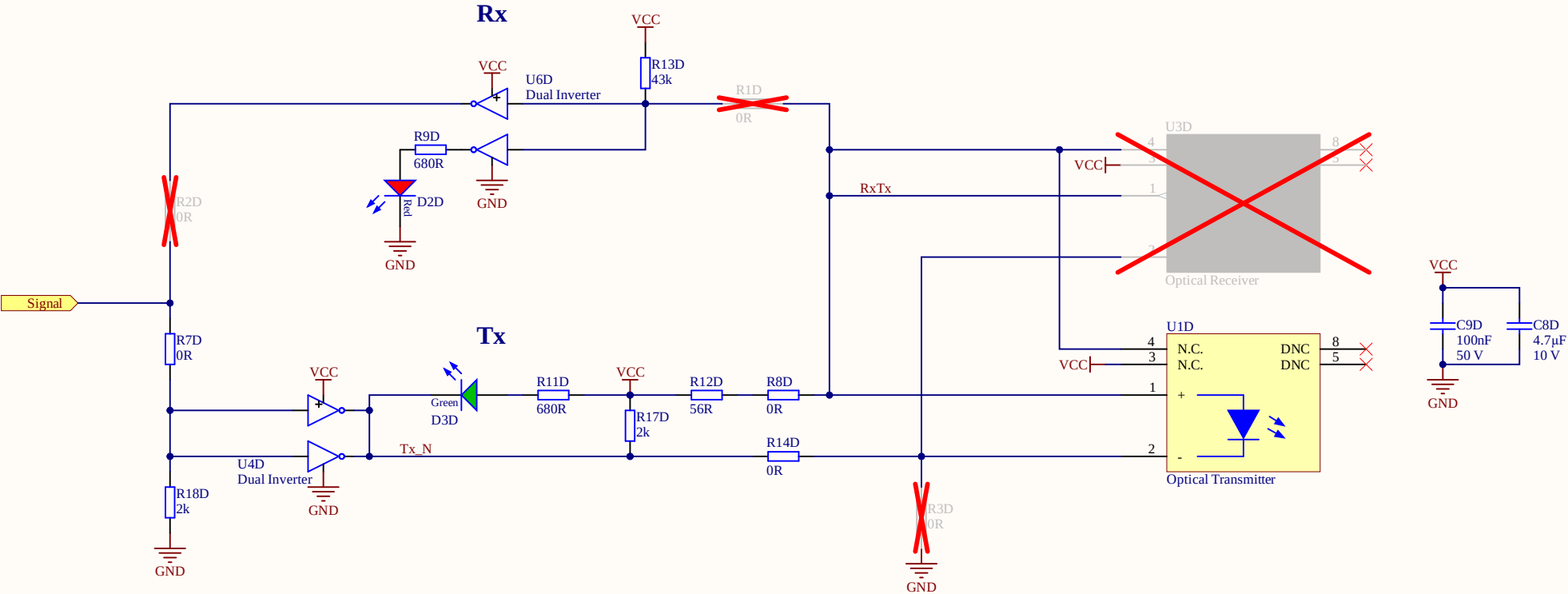

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.3 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

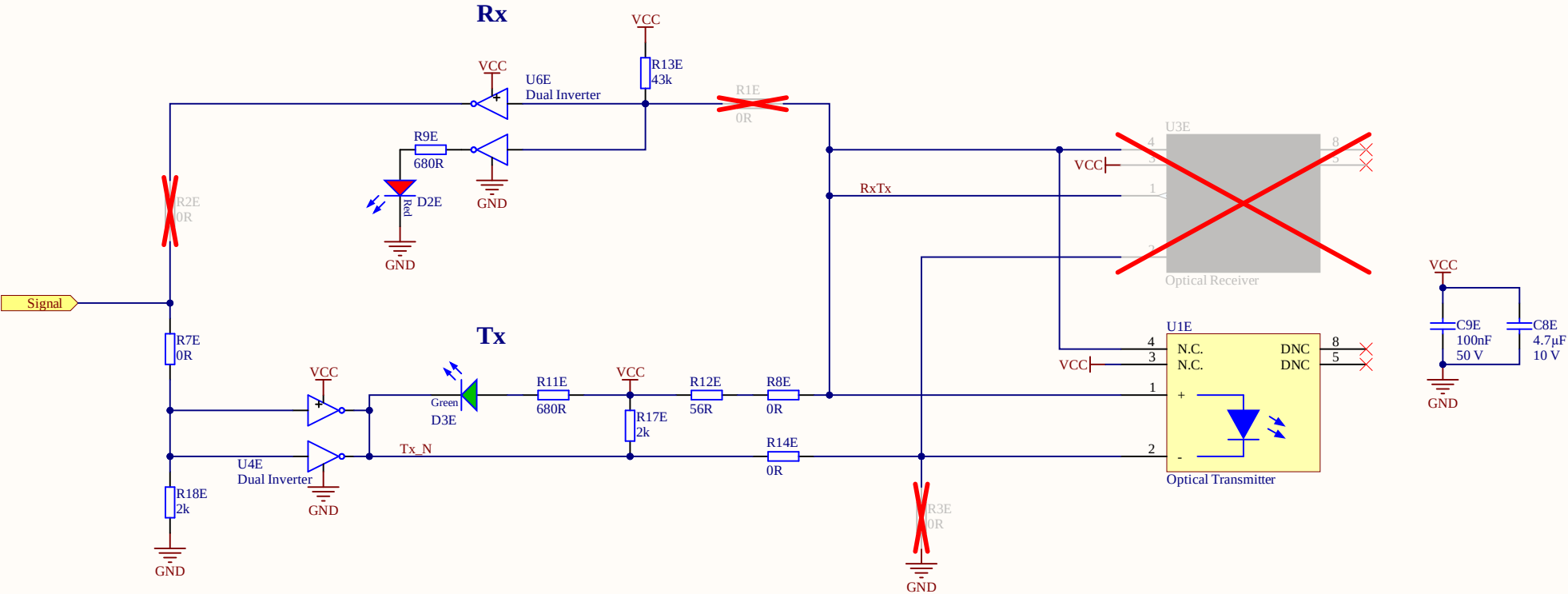


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

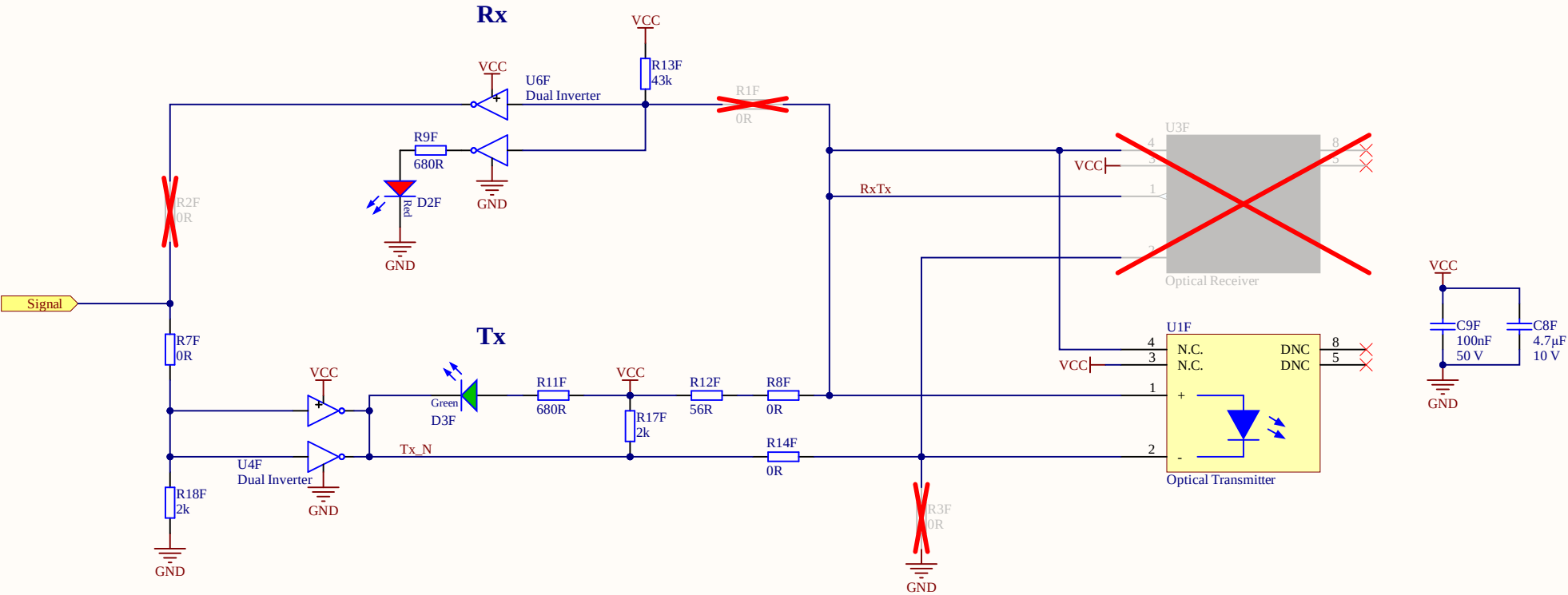


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

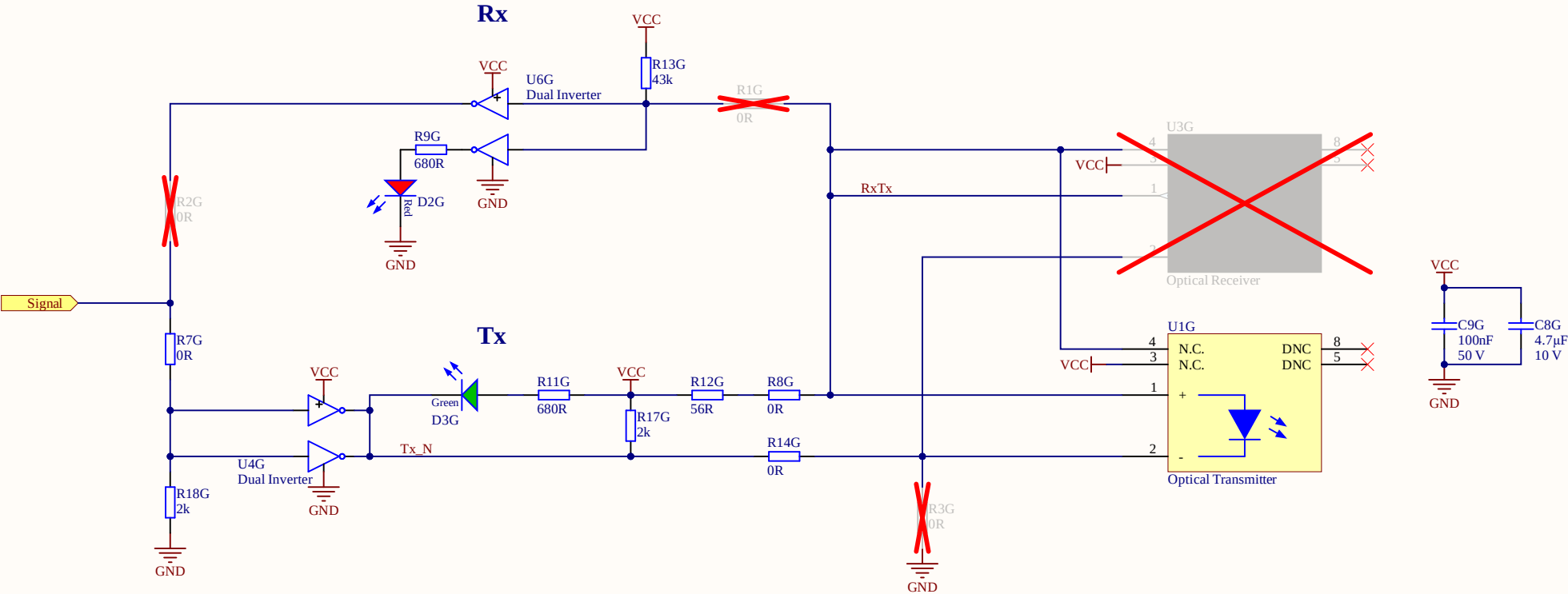

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.6 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

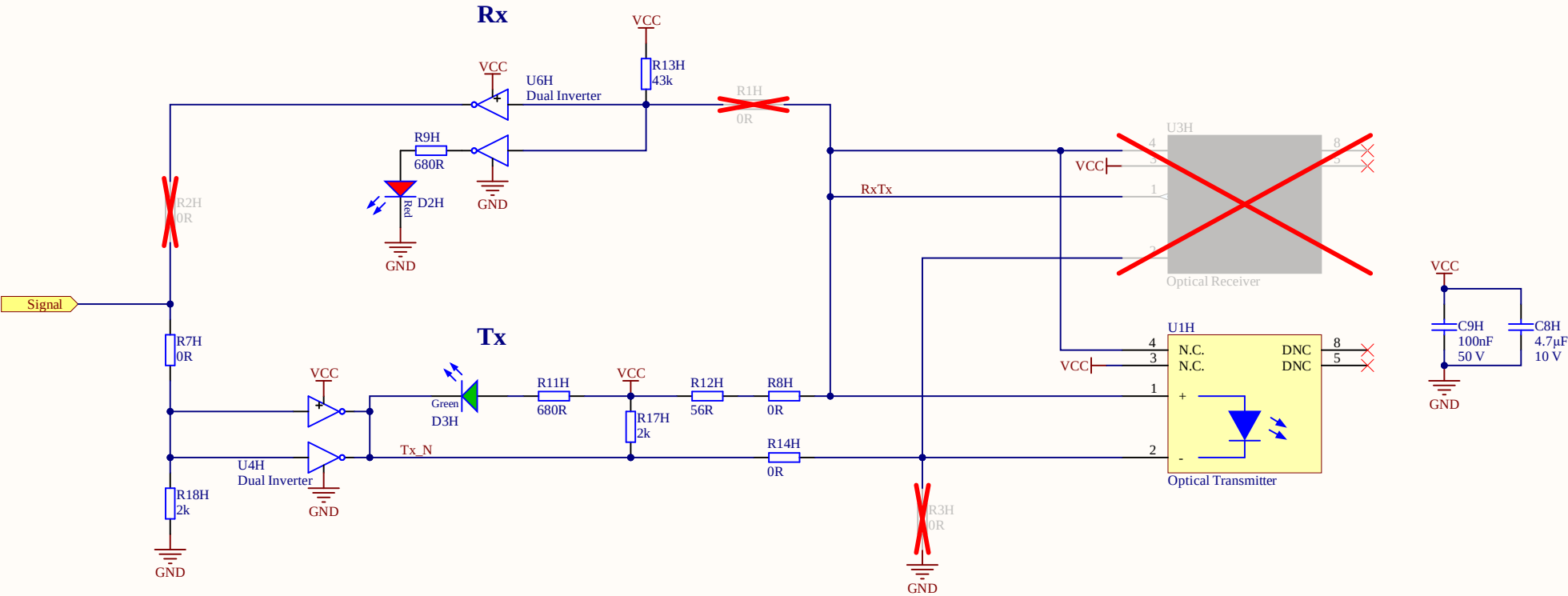


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

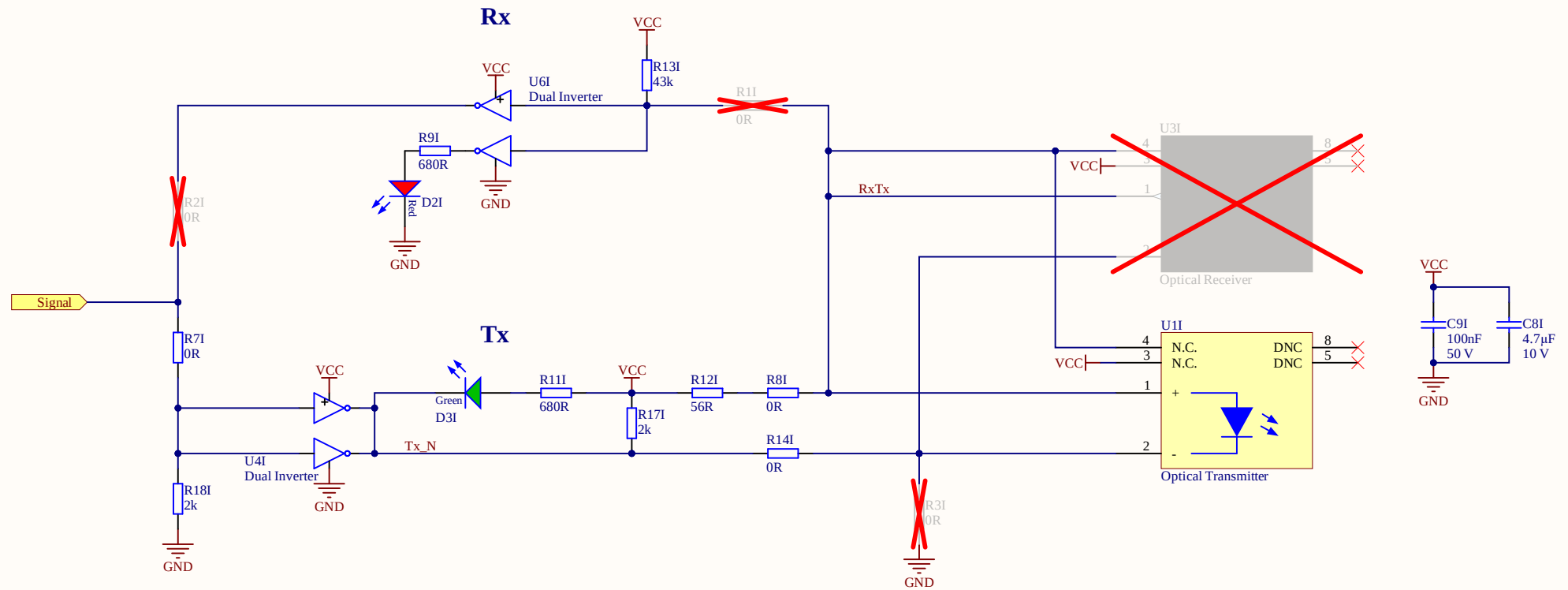


Title: Optical_RX_TX.SchDoc		
Revision: Rev08	Design Engineer: B. Kohlmann & A.Geiger	
Project: Digital_Optical.PrjPCB		
		UltraZohm www.ultrazohm.com
		Date: 21.02.2025 Sheet 4.8 of 21

Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

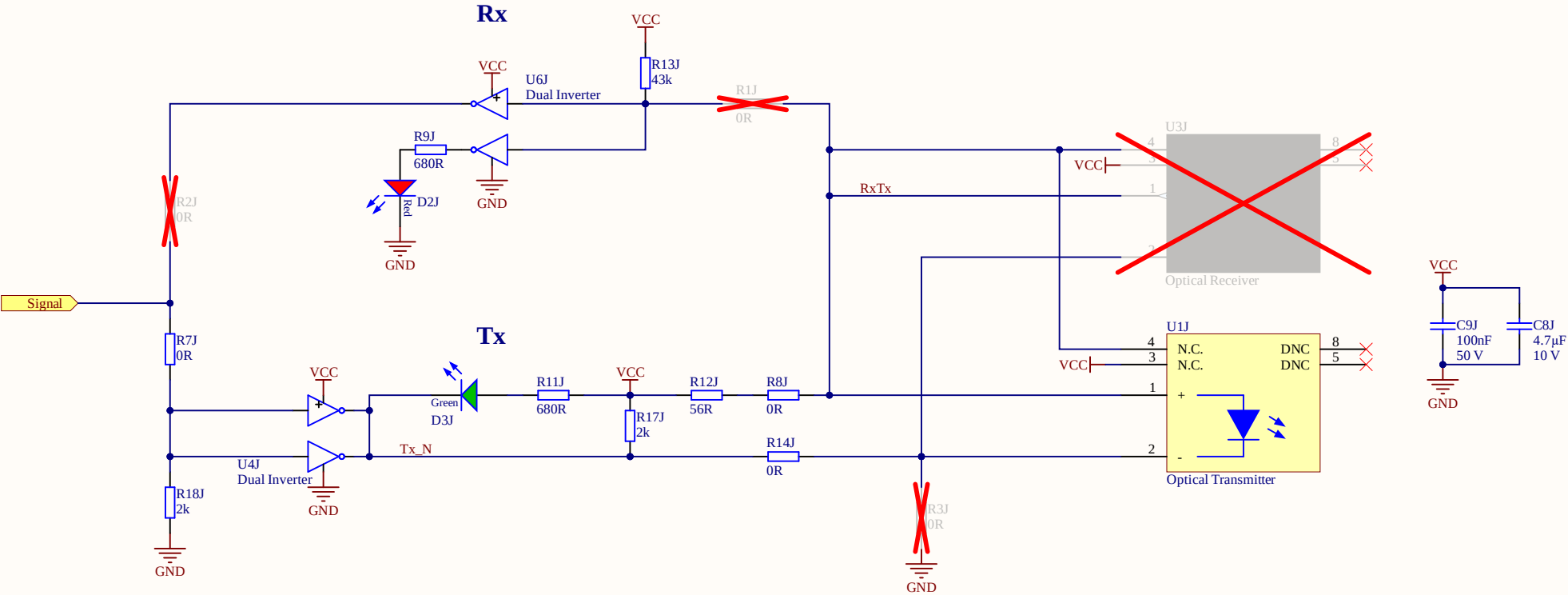


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

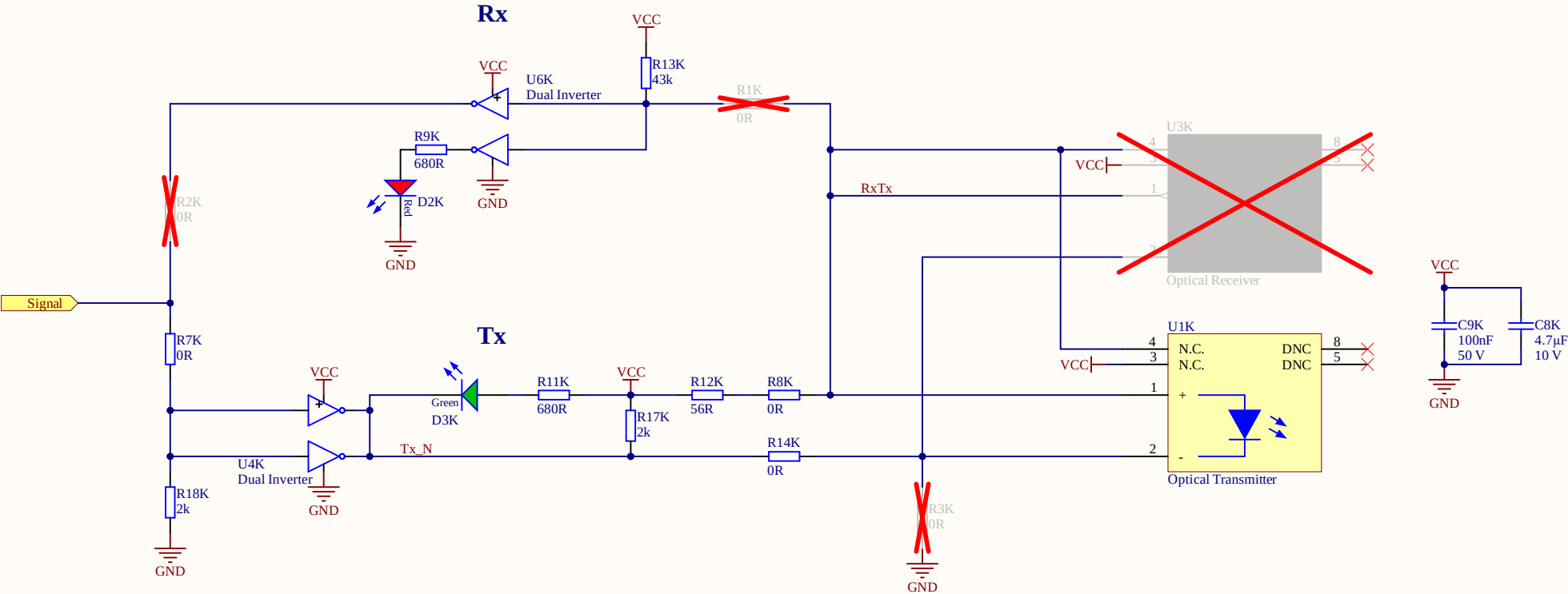


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

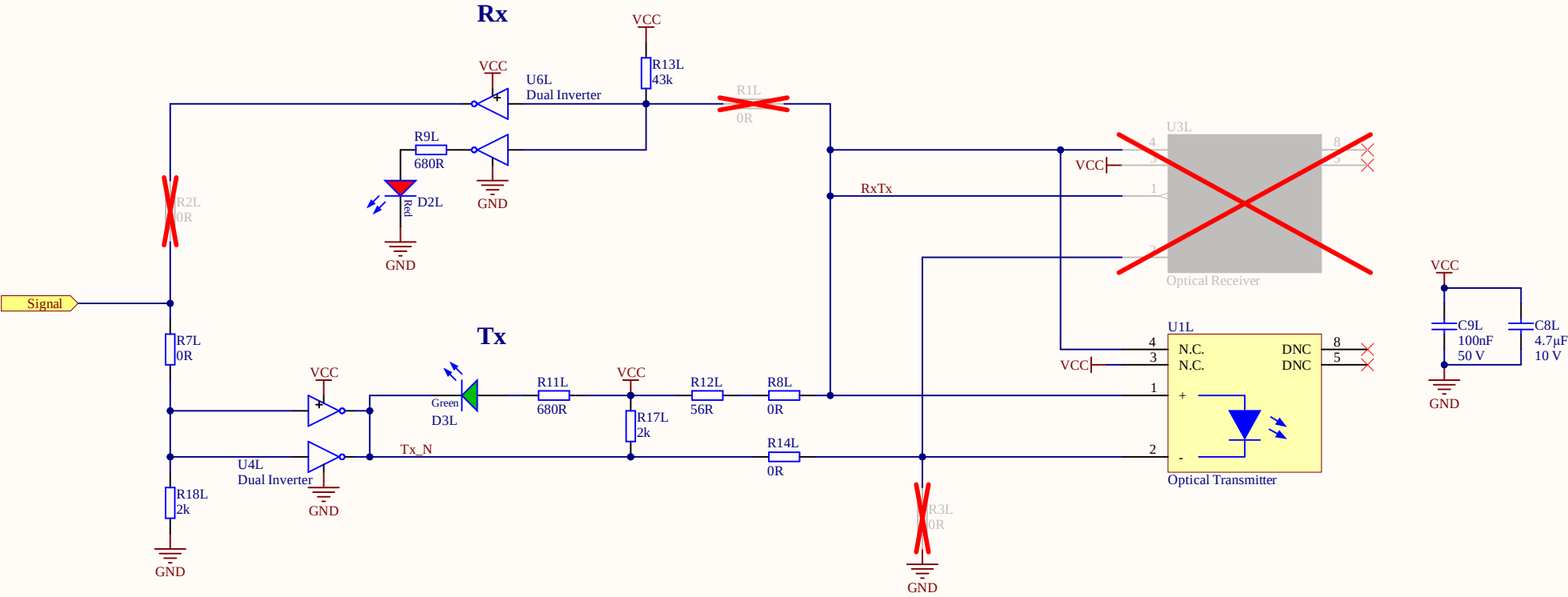

Title Optical_RX_TX.SchDoc

Revision: Rev08

Design Engineer: B. Kohlmann & A.Geiger

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 21.02.2025

Sheet 4.11 of 21




Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

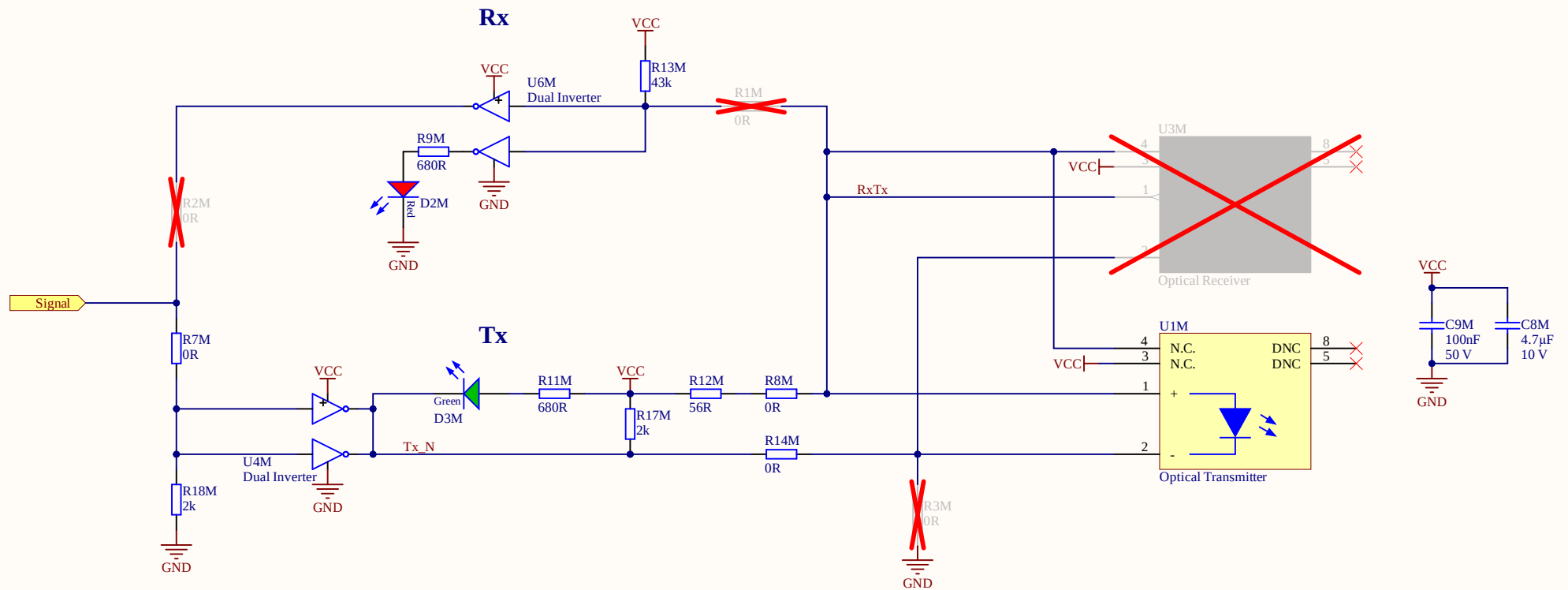


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

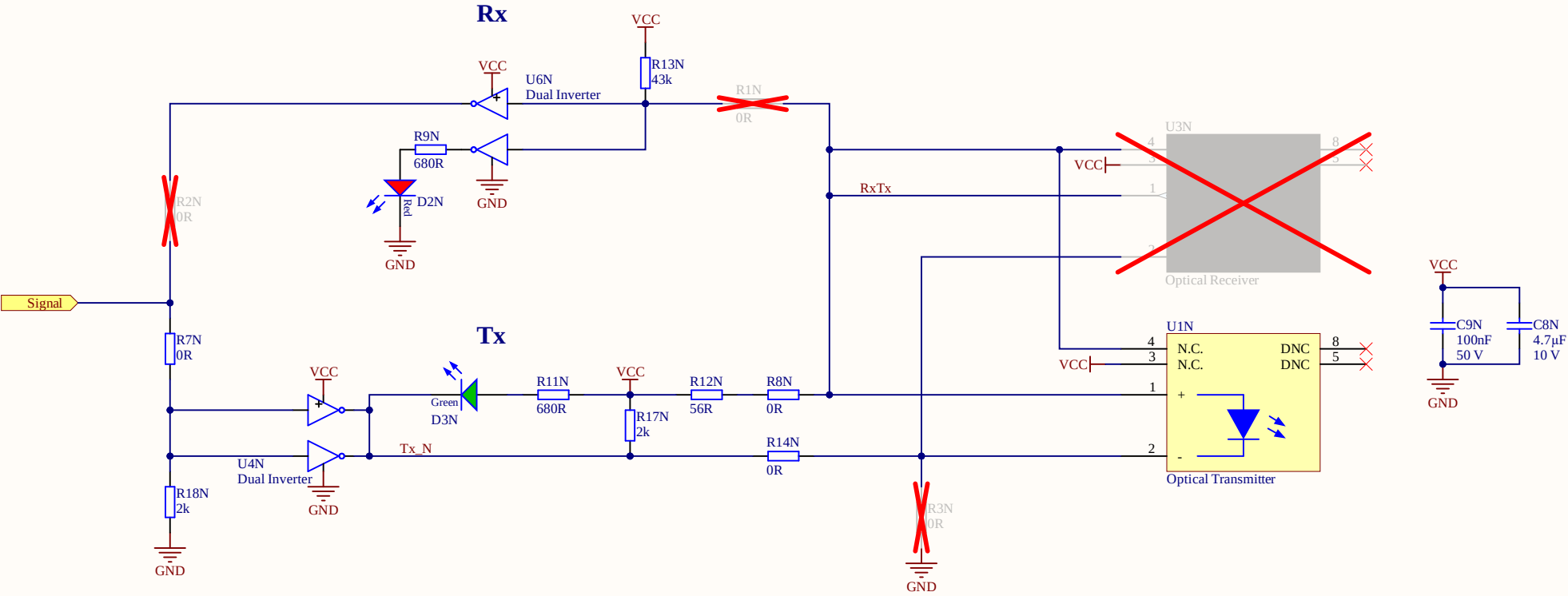


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

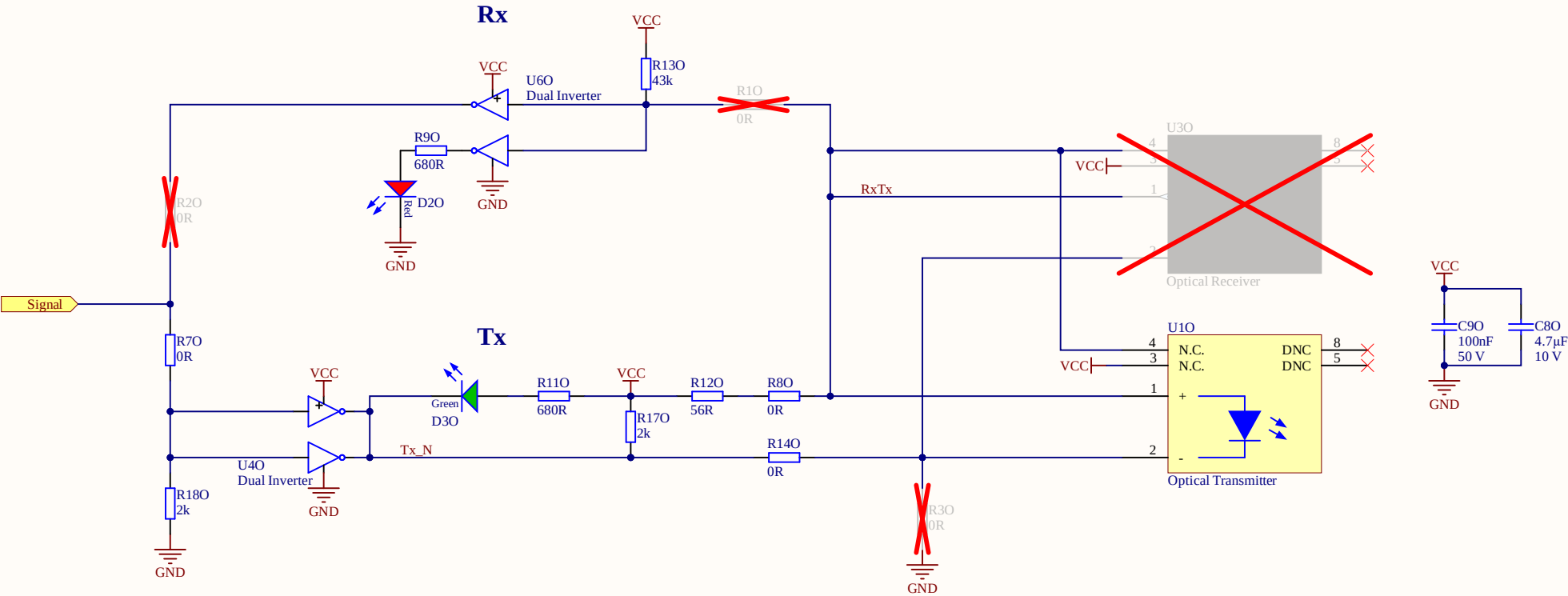


Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

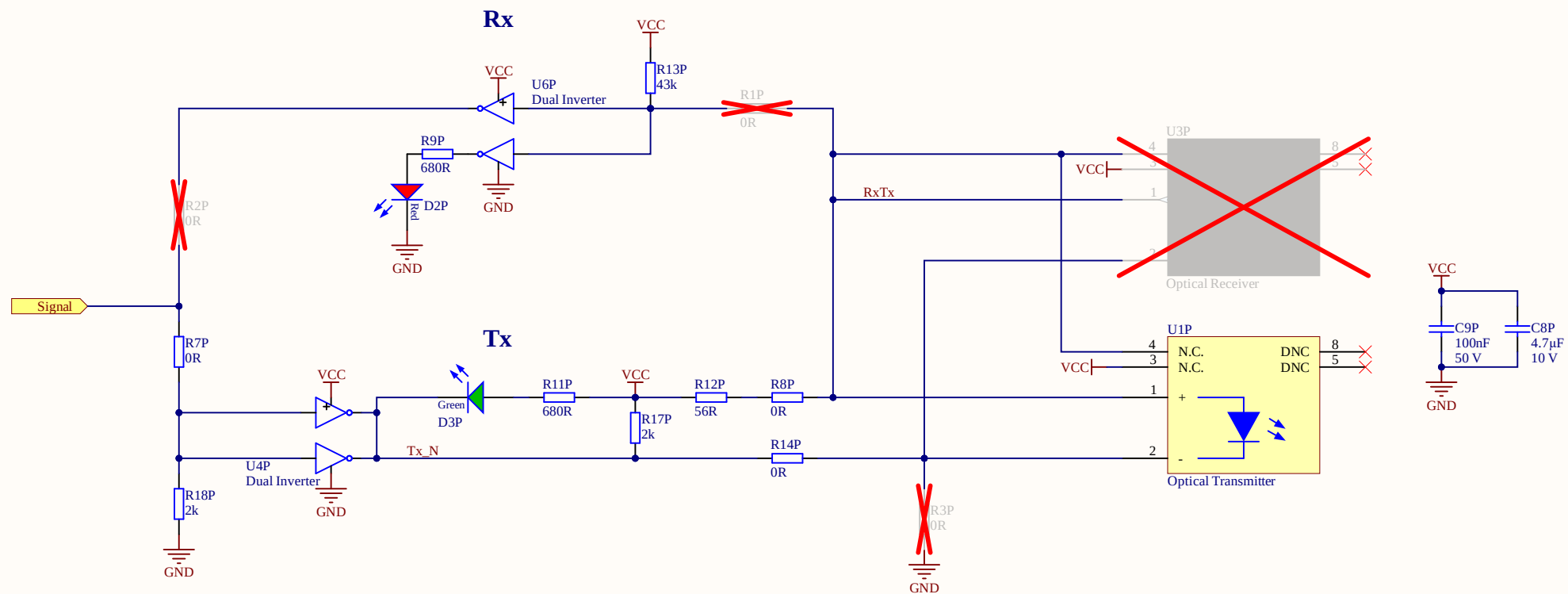


Title: Optical_RX_TX.SchDoc		 UltraZohm www.ultrazohm.com	
Revision: Rev08	Design Engineer: B. Kohlmann & A.Geiger		
Project: Digital_Optical.PrjPCB			
		Date: 21.02.2025	
		Sheet 4.15 of 21	

Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

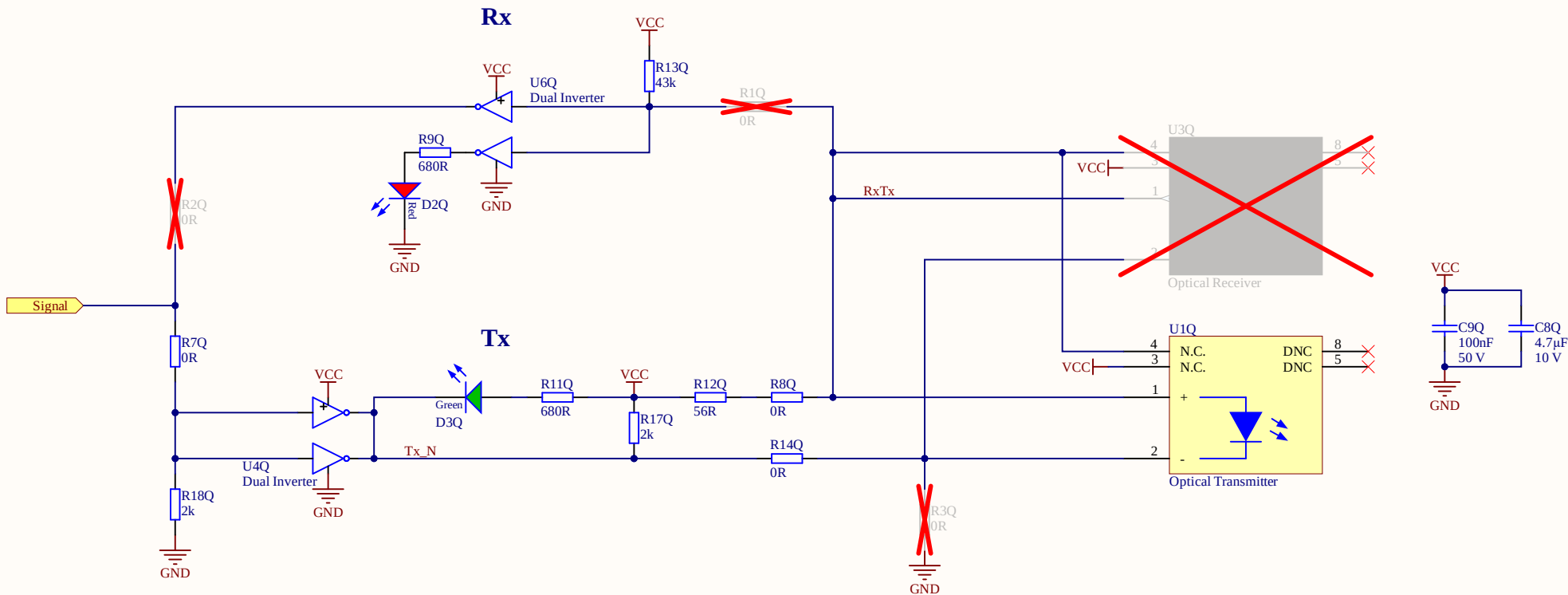

Poor Mans Table of Truth for Tx

Transmitter LED	Node Tx_N	LED D3	Signal
OFF	HIGH	OFF	LOW
ON	LOW	ON	HIGH

Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	LED D2
OFF	HIGH	OFF
ON	LOW	ON

