

Connector
CarrierConnector.SchDoc



GATE[1..14]

GATE



Repeat(TX_PWM,1,14)
Optical_TX.SchDoc



Signal[15..18]

Signal

Repeat(RX,15,18)
Optical_RX.SchDoc

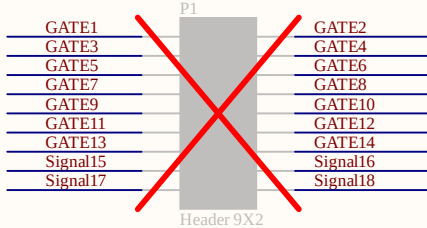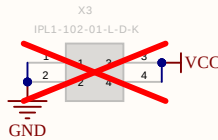

Serial1
Serial
Serialnumber 6,3 x 6.3mm


ProjectName1

Laser1
Logo Laser
Voll_Laser

LOGO1



Power
Power.SchDoc

 

Title TopSheet.SchDoc

Revision: Rev06

Design Engineer: E. Romaschenko

Project: Digital_Optical.PrjPCB



UltraZohm



www.ultrazohm.com

Date: 07.04.2021

Sheet 1 of 21



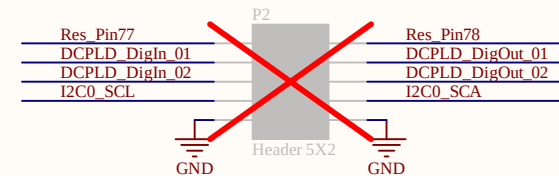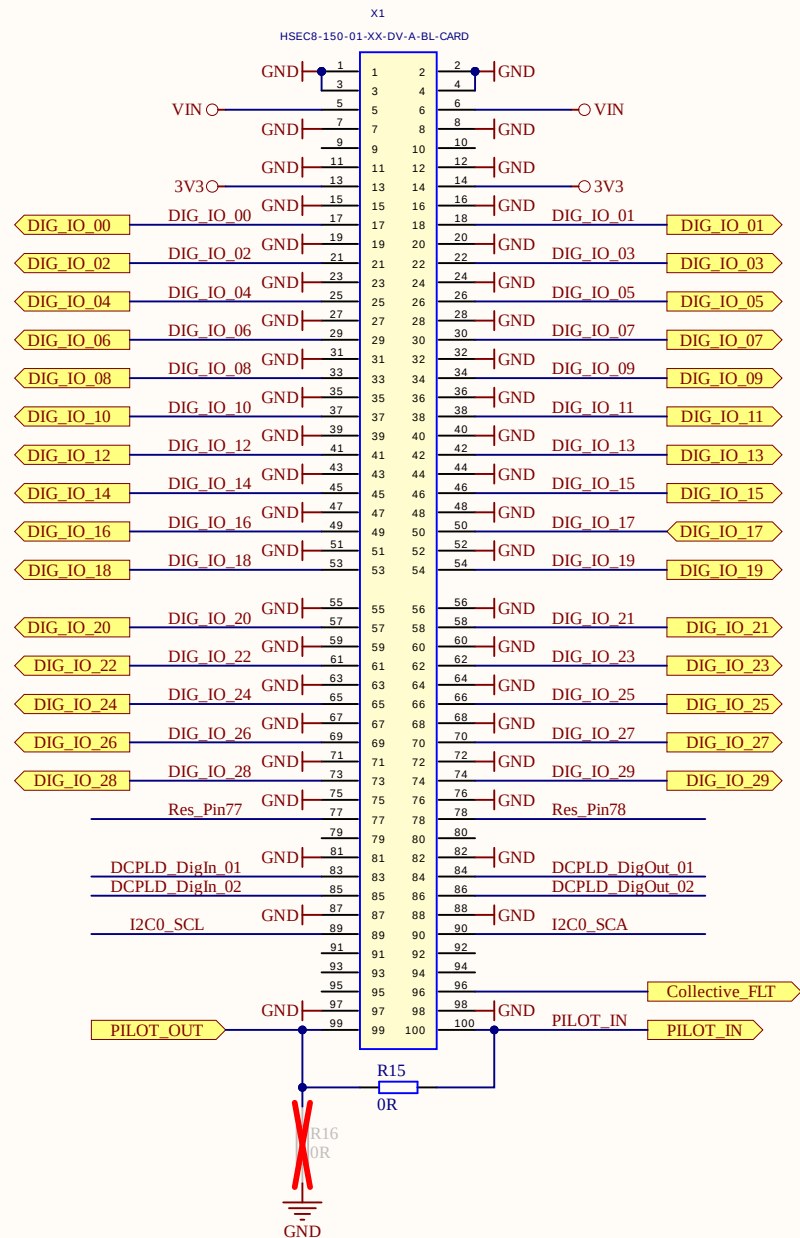

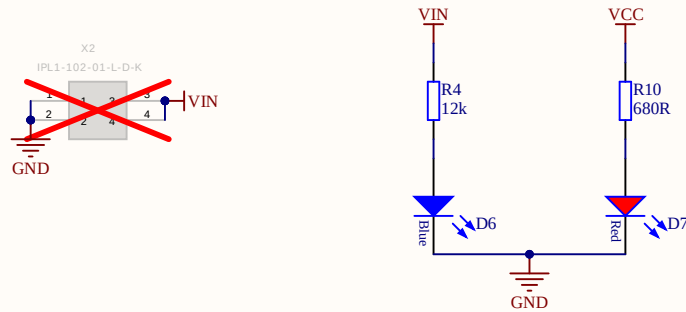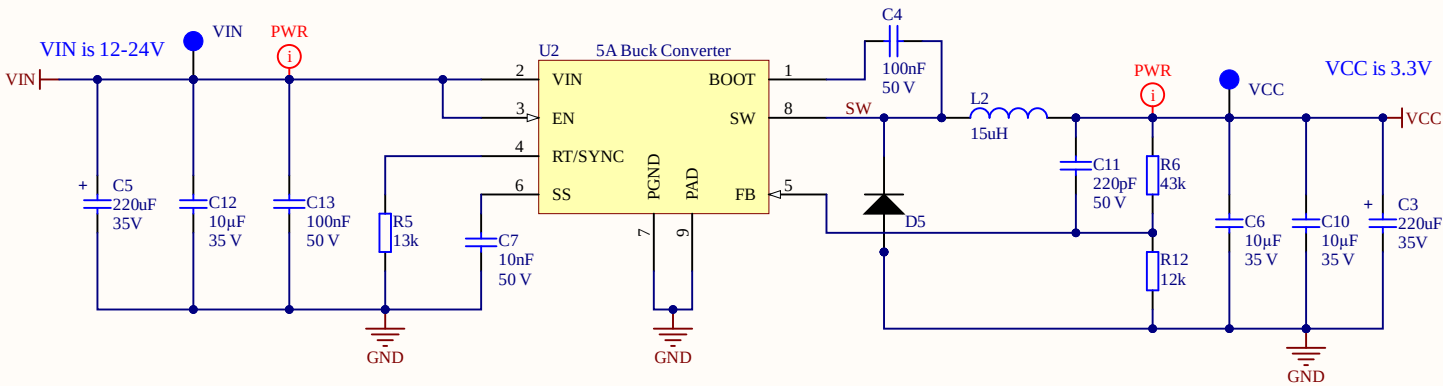


Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

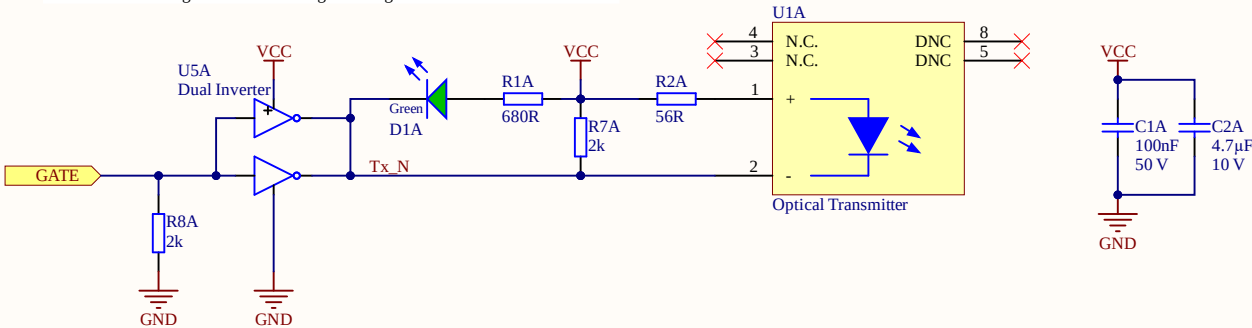With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

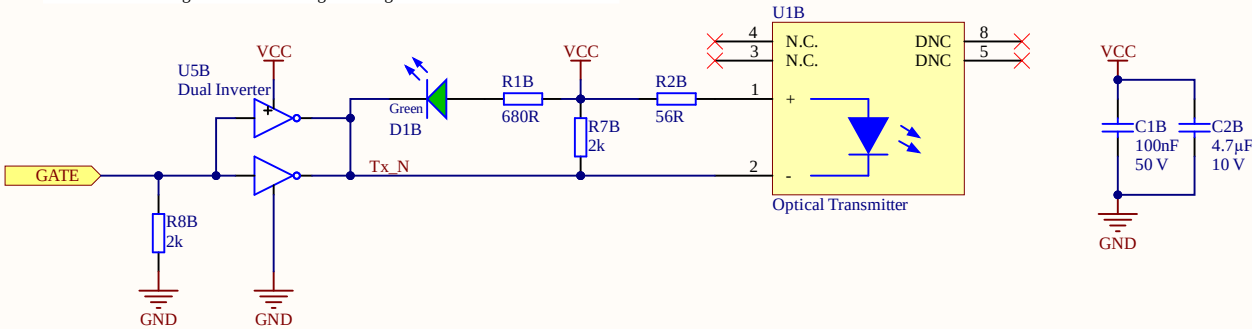With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

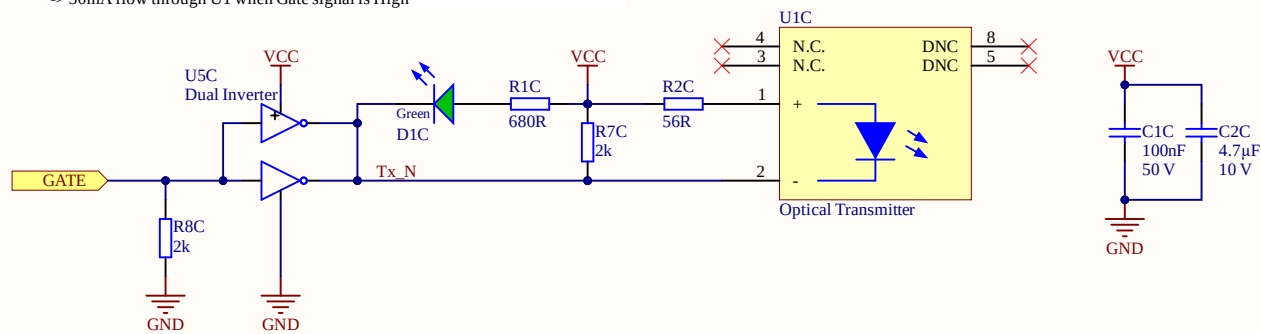With $V_{cc} = 3.3V$ and $R_2 = 56R$
 -> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

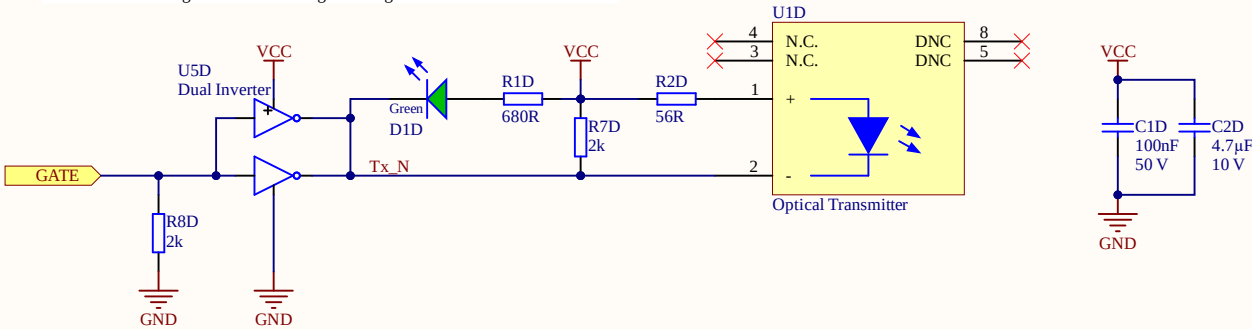With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

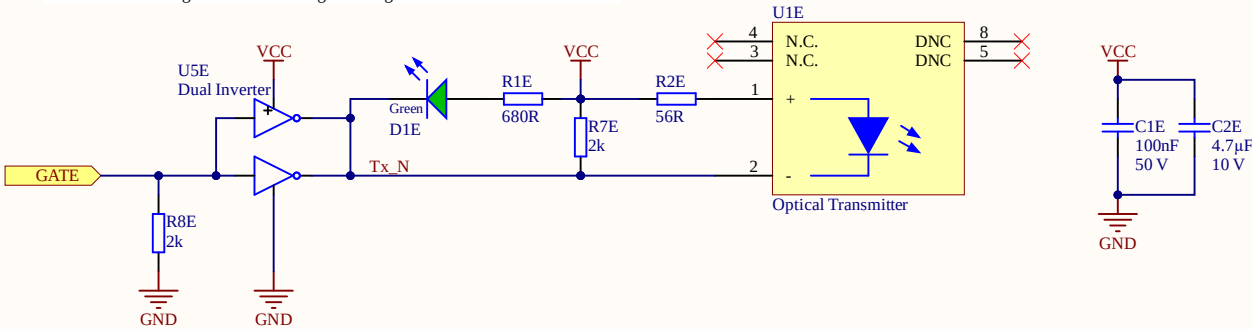With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

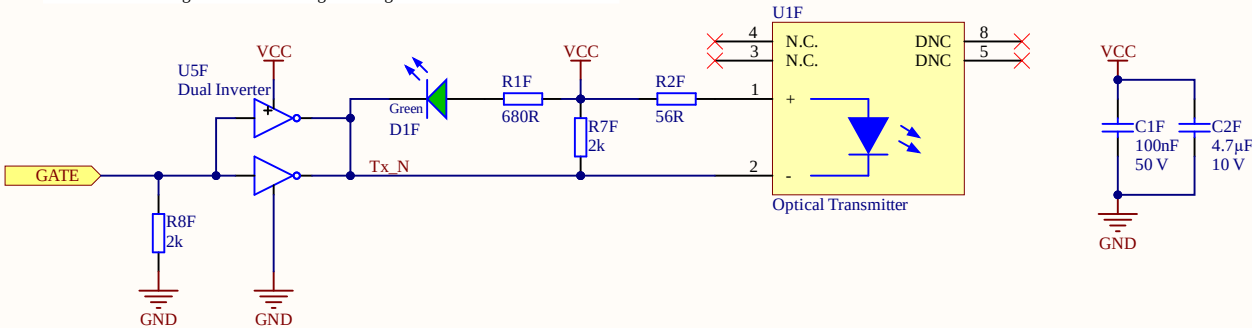With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

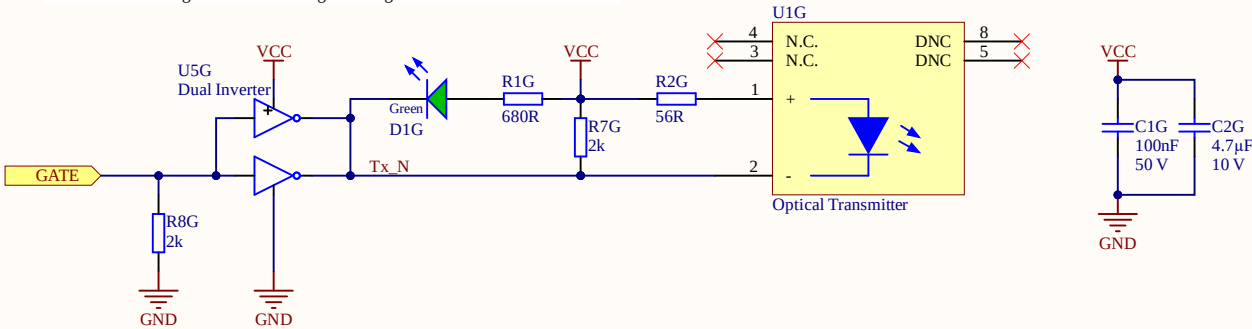With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

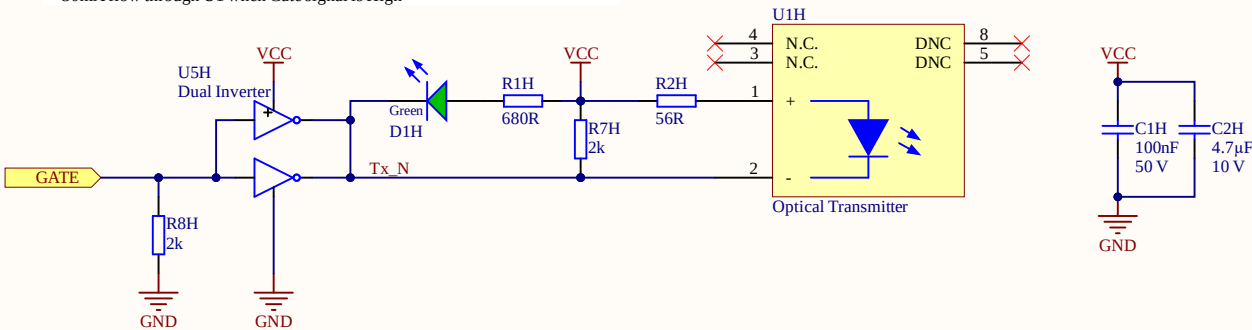With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

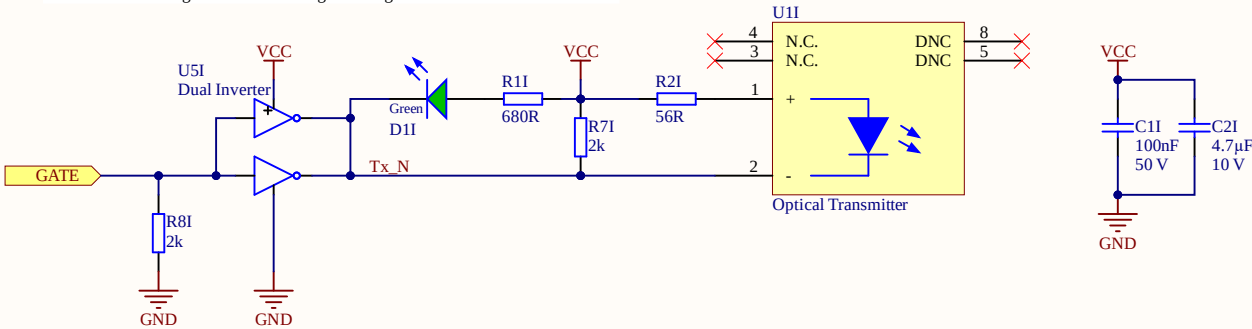With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

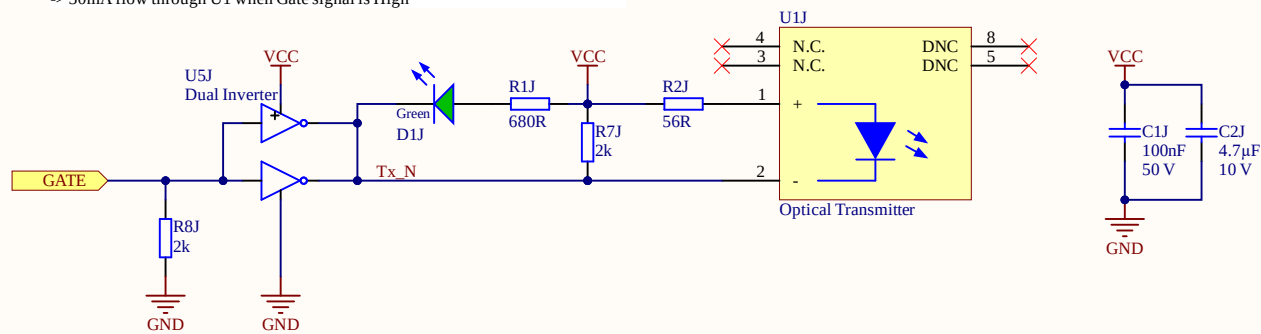With $V_{cc} = 3.3V$ and $R2 = 56R$
-> 30mA flow through U1 when Gate signal is High



Title Optical_TX.SchDoc

Revision: Rev06

Design Engineer: E. Romaschenko

Project: Digital_Optical.PrjPCB

UltraZohmwww.ultrazohm.com

Date: 07.04.2021

Sheet 4.10 of 21




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

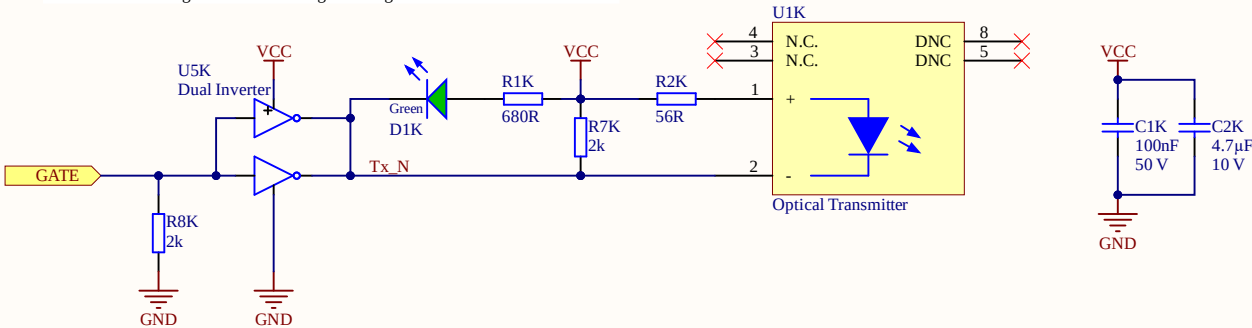With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

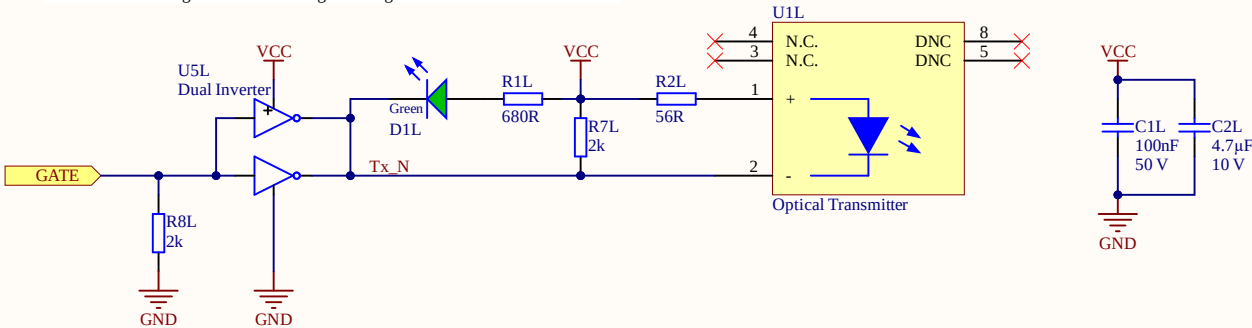With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW

maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

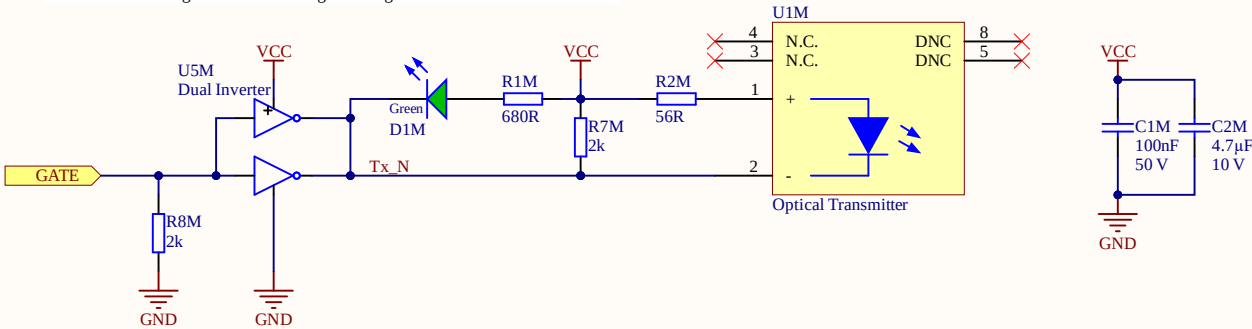With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High




Poor Mans Table of Truth for Tx

GATE	Transmitter LED	Node Tx_N
LOW	OFF	HIGH
HIGH	ON	LOW


maximum drive strength of U5 is 24mA per Channel
resulting in a total maximum drive strength of 48mA per Transmitter

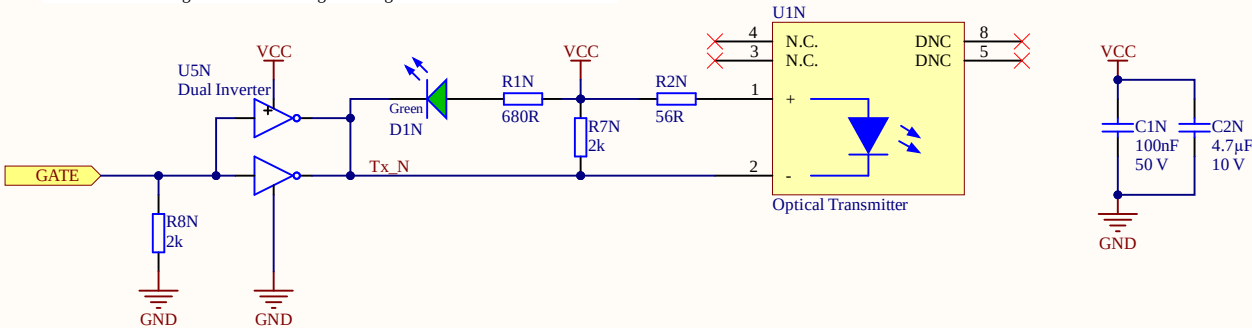With Vcc = 3.3V and R2 = 56R
-> 30mA flow through U1 when Gate signal is High



Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	Signal	Signal
OFF	HIGH	LOW	LOW
ON	LOW	HIGH	HIGH

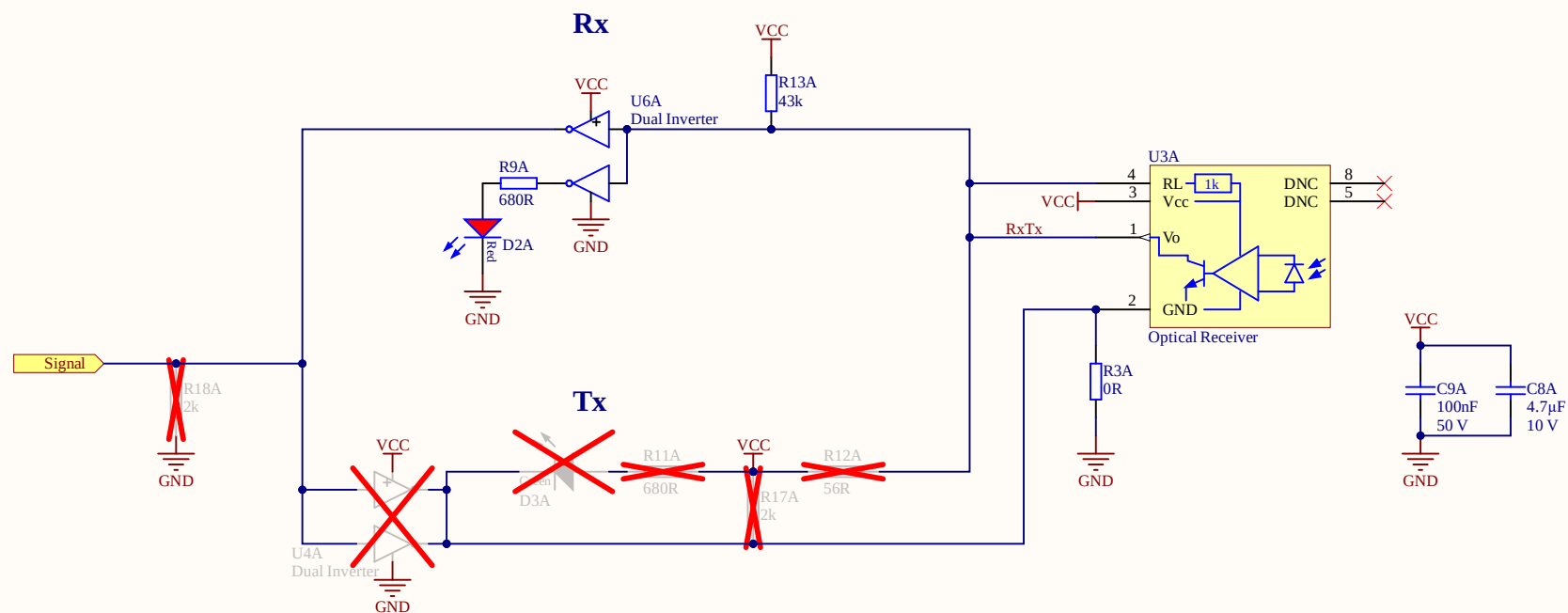


Title: Optical_RX.SchDoc	
Revision: Rev06	Design Engineer: E. Romaschenko
Project: Digital_Optical.PrjPCB	



Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	Signal	Signal
OFF	HIGH	LOW	LOW
ON	LOW	HIGH	HIGH

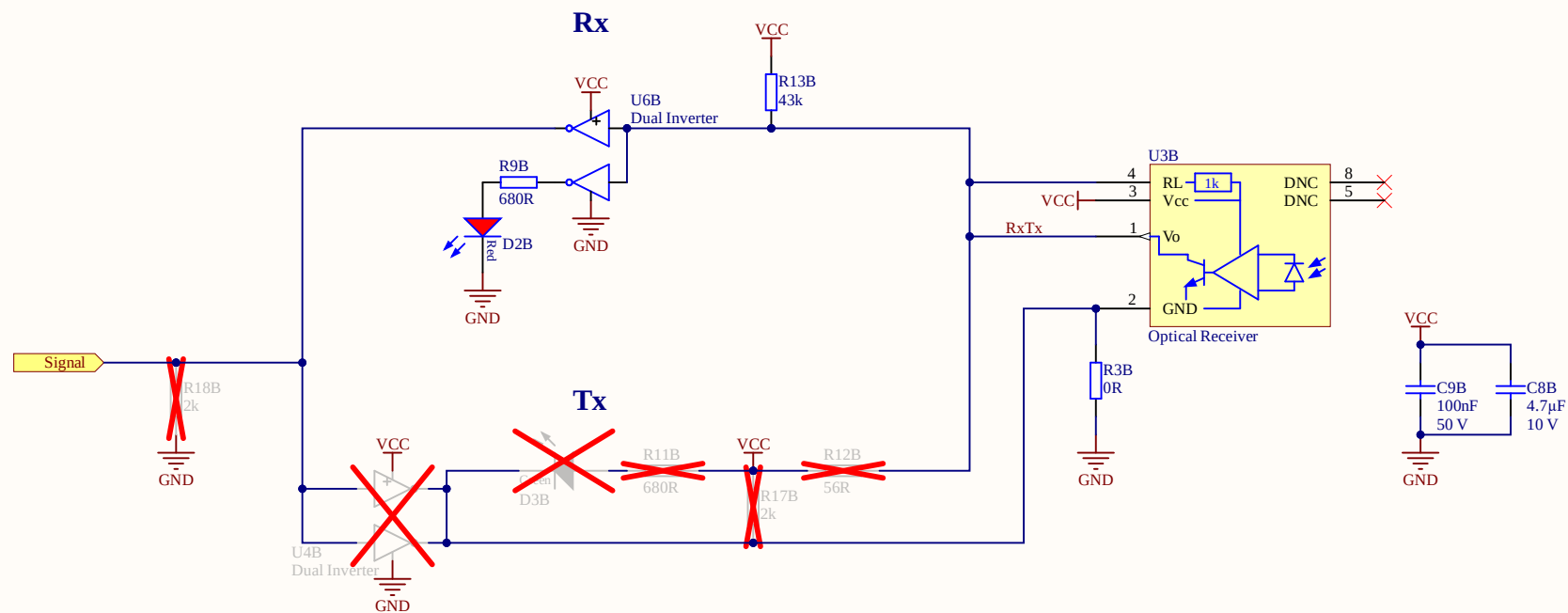

Title	Optical_RX.SchDoc
-------	-------------------

Revision: Rev06

Design Engineer: E. Romaschenko

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com


Date: 07.04.2021

Sheet 5.16 of 21



Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	Signal	Signal
OFF	HIGH	LOW	LOW
ON	LOW	HIGH	HIGH

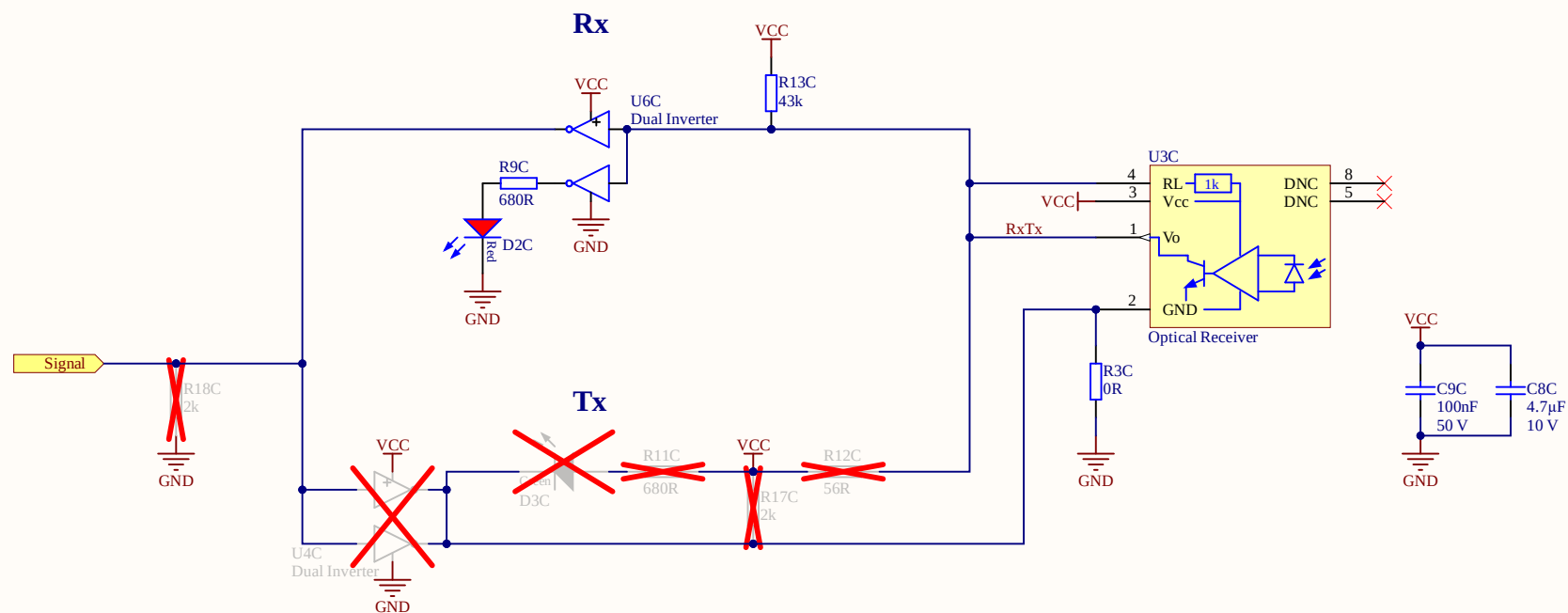

Title	Optical_RX.SchDoc
-------	-------------------

Revision: Rev06	Design Engineer: E. Romaschenko
-----------------	---------------------------------

Project: Digital_Optical.PrjPCB

UltraZohm

www.ultrazohm.com

Date: 07.04.2021

Sheet 5.17 of 21



Poor Mans Table of Truth for Rx

Receiver LED	Node RxTx	Signal	Signal
OFF	HIGH	LOW	LOW
ON	LOW	HIGH	HIGH

